

2207/302

TELECOMMUNICATION PRINCIPLES

Oct./Nov. 2018

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**DIPLOMA IN AERONAUTICAL ENGINEERING AVIONICS
(COMMUNICATION AND NAVIGATION OPTION)**

TELECOMMUNICATION PRINCIPLES

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Mathematical tables/Non-programmable scientific calculator;

Smith chart;

Drawing instruments.

Answer any FIVE of the following EIGHT questions in the answer booklet provided.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 7 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

1.

- (a) (i) List two factors considered when selecting an RF oscillator.
- (ii) With the aid of a circuit diagram, describe the operation of a tuned collector oscillator. (10 marks)
- (b) Figure 1 shows the block schematic diagram for a voltage - negative feedback amplifier. Derive the expression for the feedback factor, β . (3 marks)

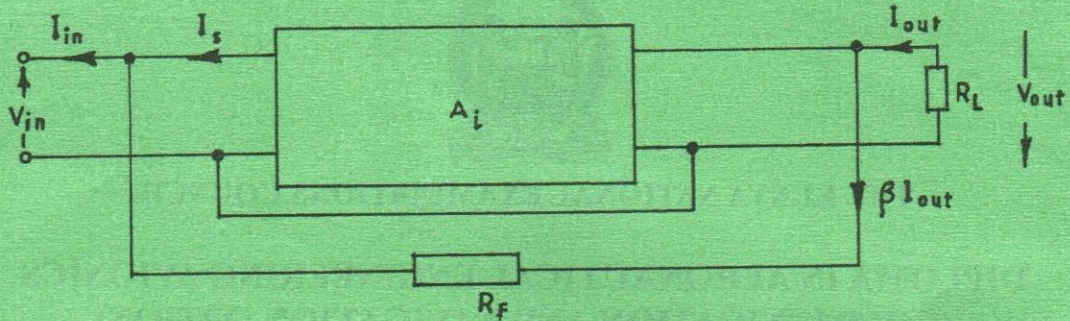


Fig. 1

- (c) An amplifier has an open loop voltage gain of 60 dB and a closed loop voltage gain of 30 dB. If the open loop gain changes to 55 dB, determine the:
- (i) feedback factor;
- (ii) new closed loop gain in dB. (7 marks)

2.

- (a) Sketch, on the same axes, the response curves for the following coupled circuits:
- (i) under-coupled;
- (ii) critically coupled;
- (iii) over-coupled. (6 marks)

- (b) A common - emitter transistor amplifier has the following hybrid parameters: $h_{ie} = 1.1 \text{ k}\Omega$, $h_{fe} = 50$, $h_{re} = 50 \times 10^{-4}$, $h_{oe} = 25 \mu\text{S}$. The source and load resistances are $1 \text{ k}\Omega$ and $10 \text{ k}\Omega$ respectively. Determine the:
- (i) current gain;
- (ii) voltage gain;
- (iii) output resistance;
- (iv) power gain. (8 marks)

- (c) A class A power amplifier draws a collector current of 30 mA at a collector voltage of 9 V. When an a.c. signal is applied, the voltage swings from 16 V to 2 V while the current swings from 40 mA to 12 mA. Determine the:
- (i) power drawn from the supply;
- (ii) output power;
- (iii) efficiency. (6 marks)

3. (a) Define each of the following with respect to silicon controlled rectifiers (SCR):

- (i) holding current;
- (ii) forward blocking region.

(2 marks)

(b) (i) Figure 2 shows a circuit diagram of an SCR - based light dimmer control. Describe its operation.

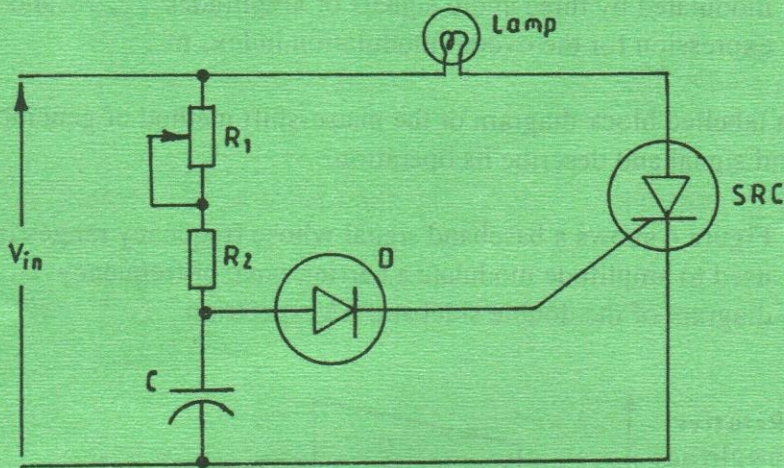


Fig. 2

(ii) With the aid of a response curve, describe the operation of a unijunction transistor. (11 marks)

(c) Figure 3 shows an input voltage, V_m , fed to a triac. The firing angle is θ while conduction angle is ϕ .

- (i) draw the output voltage waveform;
- (ii) describe the triac operation.

(7 marks)

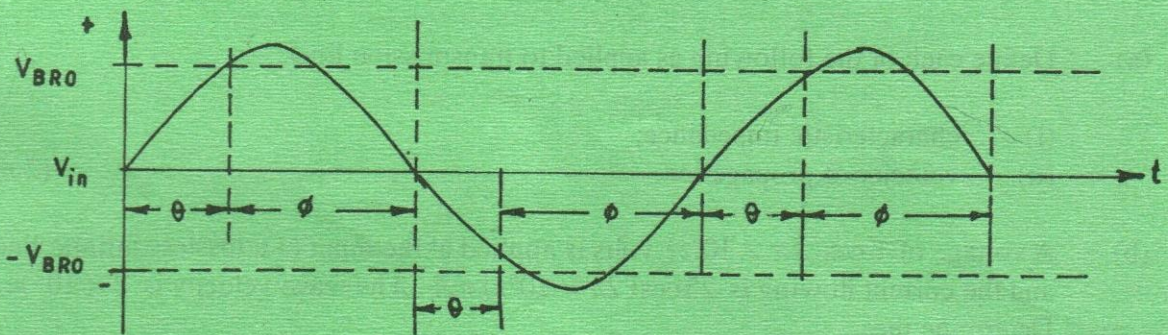


Fig. 3

0.025
0.04 - 0.02

4.

- (a) (i) Define each of the following with respect to amplitude modulation (AM) systems:
- I. efficiency;
 - II. modulation index.
- (ii) A sinusoidal carrier wave of amplitude V_C is simultaneously amplitude modulated by three audio signals of amplitudes V_1 , V_2 and V_3 . Derive the expression for the overall modulation index, m_t . (6 marks)
- (b) Draw a labelled block diagram of the phase-shift method of generating a single sideband signal and describe its operation. (6 marks)
- (c) (i) Figure 4 shows a baseband signal whose frequency ranges from f_1 to f_2 . It is used to amplitude modulate a carrier wave of frequency f_c . Draw a labelled diagram of the double sideband AM spectrum.

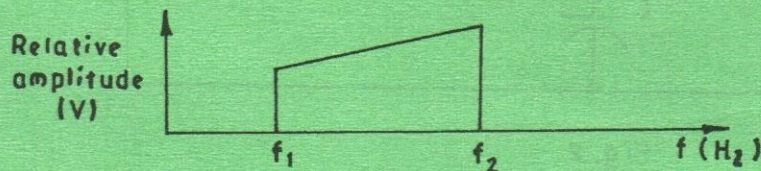


Fig. 4

- (ii) The output power of a DSB AM signal is 150 kW when the depth of modulation is 0.78. Determine the:
- I. carrier power;
 - II. power of each sideband. (8 marks)

5. (a) Define each of the following as applied to transmission lines:

- (i) characteristic impedance;
- (ii) velocity of propagation. (2 marks)

(b) A voltage of $6 \cos(2\pi \times 10^6 t)$ volts is applied at the input of a lossless infinite line and the current flowing is $25 \cos(2\pi \times 10^6 t)$ mA. The wave velocity is 2×10^8 m/s. Determine the:

- (i) characteristic impedance;
- (ii) signal wavelength. (4 marks)

(c) A transmission line has a characteristic impedance of 600Ω and is terminated by a load of $300 + j450 \Omega$. Using the Smith Chart, determine the:

- (i) voltage standing wave ratio;
- (ii) magnitude and phase angle of the reflection coefficient. (8 marks)

(d) With the aid of a circuit diagram, describe the operation of a discrete component monostable multivibrator. (6 marks)

6. (a) (i) List any **two** telecommunication services that use Pulse Code Modulation (PCM).
- (ii) Figure 5 shows a block diagram of a pulse modulating system.
- I. Describe its operation.
 - II. Draw the waveforms at points 1, 2 and 3. (11 marks)

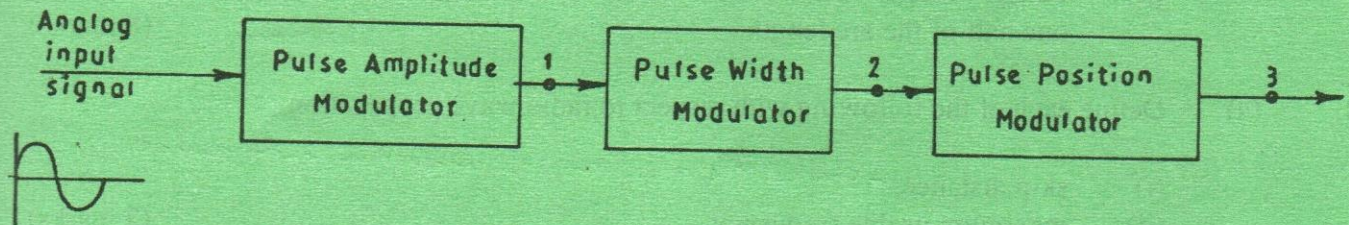


Fig. 5

- (b) (i) With the aid of a circuit diagram, describe the operation of a silicon diode clipper whose sinusoidal input is $10V$ and output is $\pm 7.7V$.
- (ii) Draw the output waveform for the clipper in (b)(i). (7 marks)
- (c) Sketch the ideal response curve of a bandpass filter. (2 marks)

7. (a) (i) List any **two** advantages of closed-loop-over open loop control systems.
- (ii) With the aid of a labelled diagram, describe the operation of an E-I displacement transducer. (9 marks)

- (b) Figure 6 shows a circuit diagram of an a.c. servomotor. Describe its operation. (3 marks)

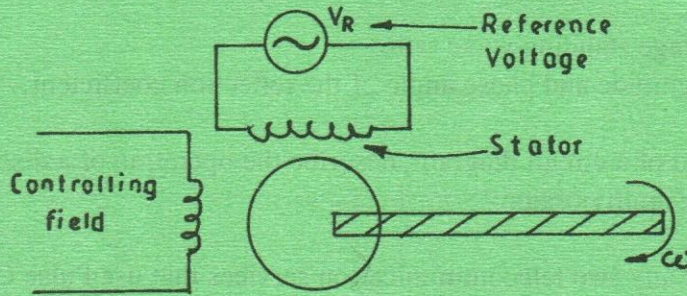


Fig. 6

- (c) A $120\text{ k}\Omega$ potentiometer with an arc length of 300° is connected to a 12 V d.c supply. Determine the:
- potentiometer constant in volts/radian;
 - output voltage when a load of $80\text{ k}\Omega$ is connected to the slider which is set at one half of the arc length. (8 marks)

8. (a) Define each of the following with respect to radio wave propagation:
- skip distance; - Shortest distance from the required on earth surface
 - maximum usable frequency. - (2 marks)

(b) Table 1 shows data for a space wave communication link.

1/2π cot


- Plot the response curve.
- Determine the:
 - received signal strength at 45 km ;
 - distance at which the signal strength is 20 mV . (7 marks)

Table 1

Distance (km)	0	10	20	30	40	50	60	70	80
Signal strength (mV)	35	47.5	33	45	22.5	35	15	25	5

- (c) (i) With the aid of a labelled diagram, describe surface duct with respect to ground wave propagation.
- (ii) The electron density of the F_1 layer of the ionosphere is 2.8×10^{12} electrons/ m^3 at a virtual height of 250 km . Determine the:
- critical frequency;
 - maximum usable frequency. $\sim \frac{f_c}{\cos \theta}$ (11 marks)

IMPEDANCE OR ADMITTANCE COORDINATES

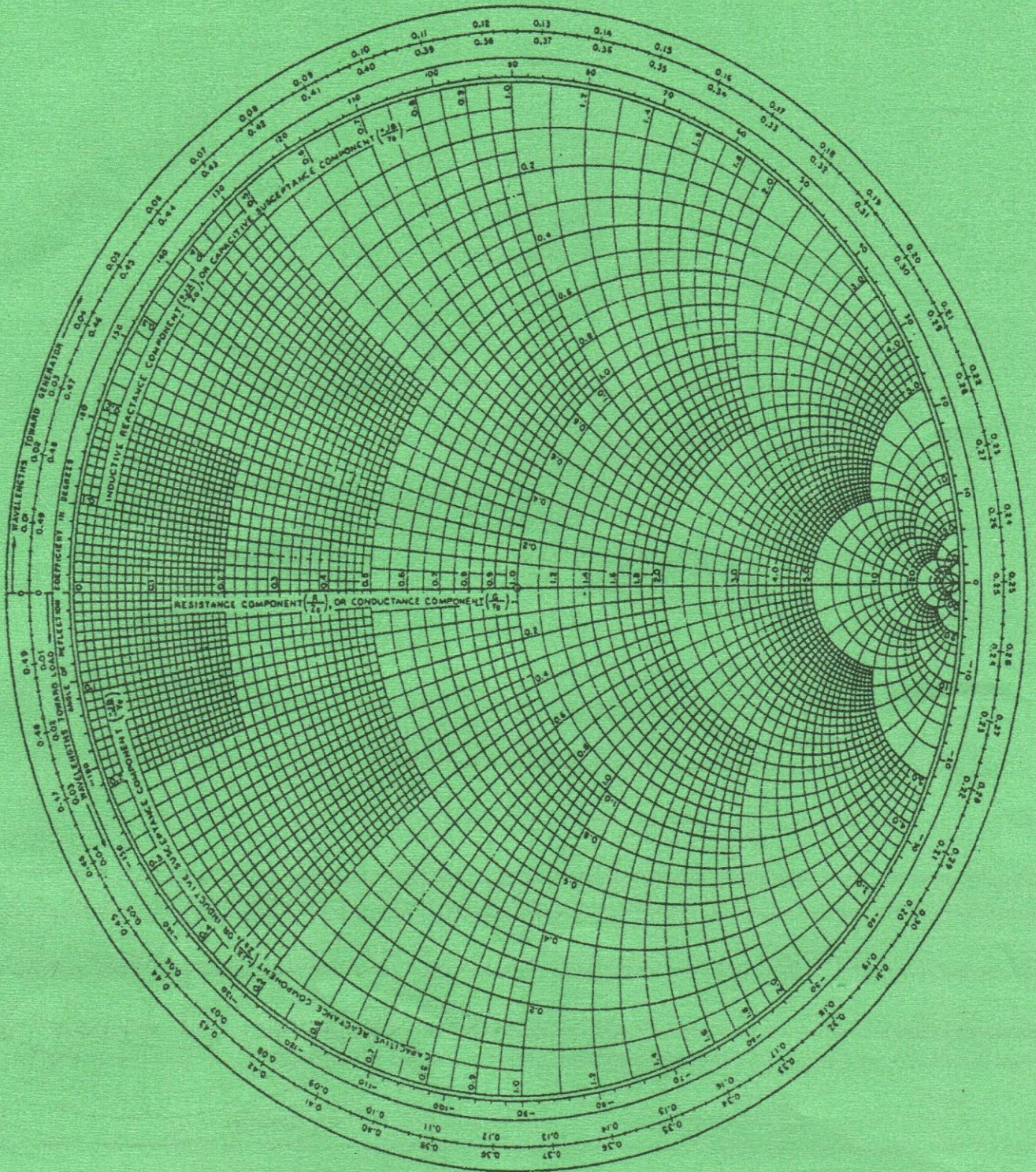

THIS IS THE LAST PRINTED PAGE.