

2207/304

DIGITAL PRINCIPLES AND MICROPROCESSORS

Oct./Nov. 2019

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**DIPLOMA IN AERONAUTICAL ENGINEERING AVIONICS
(COMMUNICATION AND NAVIGATION OPTION)**

DIGITAL PRINCIPLES AND MICROPROCESSORS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Non programmable scientific calculator;

8080/8085 Instruction set;

Drawing instruments.

*Answer **FIVE** of the **EIGHT** questions in the answer booklet provided.*

All questions carry equal marks.

Maximum marks for each part of a question are as shown.

Candidates should answer the questions in English.

This paper consists of 7 printed pages.

**Candidates should check the question paper to ascertain that
all the pages are printed as indicated and that no questions are missing.**

① (a) Convert the decimal number 22.34375_{10} into:

- (i) binary;
- (ii) octal;
- (iii) hexadecimal.

(7 marks)

(b) Evaluate each of the following in the given bases:

(i)
$$\frac{(FD\ 16)_{16}}{(CE\ 2F)_{16}}$$

(ii) $(1001_2 - 1110_2)$ using 8-bits, two's complement.

17
* (iii) $111_2 \times 101_2$.

(7 marks)

(c) (i) Convert the decimal number 367_{10} into:

- (I) 8-4-2-1 BCD code;
- (II) EXcess-3 code.

(ii) Convert the binary number 101110_2 into gray code.

(6 marks)

② (a) For a two input XOR gate, draw its:

- (i) truth table;
- (ii) logic symbol.

(4 marks)

(b) (i) State the following Boolean laws for three variables, A, B and C:

- (I) associative;
- (II) distributive.

% (ii) Simplify the following Boolean expression using De'Morgan's theorem:

$$Q = \overline{X\overline{Y}(X+Z)}$$

(7 marks)

(c) A logic circuit is required to monitor three elevators A, B and C. Anytime at least two of the three elevators are at ground level, a logic 1 at the output of the circuit triggers an alarm, Q. By taking logic 1 to represent elevator at ground level.

- (i) draw a truth table representation of the system;
- (ii) with the aid of a K-map, obtain a simplified Boolean expression for the elevators control;
- (iii) implement the expression in c (ii) using NAND gates only.

(9 marks)

3. (a) Define each of the following as used in flip-flops:

- (i) set up time;
- (ii) level triggered;
- (iii) propagation delay.

(3 marks)

(b) With the aid of a logic diagram and truth table, explain the following as used in RS flip-flops:

- (i) no change;
- (ii) set;
- (iii) invalid conditions.

(8 marks)

(c) With the aid of a logic diagram and truth table, explain the implementation of JK flip-flop using RS flip-flop and NAND gates.

(9 marks)

4. (a) (i) State **two** applications of shift registers.

(ii) Figure 1 shows a 4-bit register.

 


Fig.1

The flip-flops are reset at the beginning and the binary data value 1011_2 is fed into the input. Draw the timing waveforms to show the states of the flip-flops after 1, 2, 3 and 4 clock pulses.

(7 marks)

(b) (i) Explain **one** advantage of synchronous counters over asynchronous counters.

(ii) Draw a schematic diagram representation of a MOD-6 asynchronous counter with active - high clock pulses using J - K flip-flops.

(6 marks)

(c) A binary counter is needed to divide a 128 kHz square signal to a 4 kHz square signal. Determine the:

- (i) modulus number of the counter;
- (ii) frequency at the second flip-flop;
- (iii) count after 132 pulses.

(7 marks)

5.

(a) State:

- (i) **two** types of parity in a data word;
- (ii) **one** logic gate used to generate parity bits.

(3 marks)

(b) Figure 2 represents a logic circuit diagram.

 


Fig. 2

- (i) draw its truth table;
- (ii) write down the Boolean expression for the outputs X and Y;
- (iii) identify the operation performed by the circuit.

(7 marks)

- (c) (i) State **three** applications of decoders;
- (ii) A function $f(A, B, C) = \sum(0, 1, 3, 7)$.

- (I) Draw the truth table for the function.
- (II) Implement the function using a decoder and a gate.

(10 marks)

6.

- (a) (i) State **three** application areas of Digital Analogue Converters (DAC).
- (ii) Draw a circuit diagram of an OP-Amp based 4-bit weighted-resistor network DAC.
- (iii) Write down the expression for the output voltage for the DAC in (a) (ii).

(7 marks)

(b) A 4-bits digital to analogue converter (DAC) has an output voltage of 8 V when the digital input is 1000_2 . Determine the:

- (i) output voltage when the digital input is 1011_2 ;
- (ii) percentage resolution.

(4 marks)

- (c) Table 1 shows an hexadecimal machine language program for 8085 microprocessor:

Table 1

Memory Address	OP CODE Hex
2000	21
2001	30
2002	F2
2003	11
2004	D0
2005	23
2006	46
2007	1A
2008	77
2009	78
200A	12
200B	76

- (i) di-assemble the program into 8085 mnemonics.
(ii) state what the program accomplishes.

(9 marks)

7.

- (a) State the function of each of the following microprocessor registers and indicate their typical sizes in bits:

- (i) accumulator;
(ii) instruction register;
(iii) stack pointer.

(6 marks)

- (b) With the aid of a flow chart, write an assembly language program to sum five bytes stored in consecutive memory locations starting from 5001 H and store the results in memory location 500 A H.

(9 marks)

- (c) A memory is organized as $4 K \times 16$. Determine the:

- (i) number of memory locations; $4 K$
(ii) number of bits in each word; 16
(iii) total number of bits in the memory. $4 K \times 16$

8. (a) State:

(5 marks)

- (i) **three** functions of an input-output (I/O) interface;
(ii) **two** sources of interrupts in a computer.

(5 marks)

(b) Describe the following input-output techniques:

- (i) programmed;
- (ii) interrupt driven.

(4 marks)

(c) Draw a flow chart for a logical fault tracing method in a microprocessor based system.

(7 marks)

(d) State the symptom(s) for each of the following faults in a microcomputer:

- (i) reset pin is permanently grounded;
- (ii) $\text{IO}/\overline{\text{M}}$ stuck to logic 0.

(4 marks)

OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC
00	NOP	28	DCX H	56	MOV D,M	81	ADD C	AC	XRA H	D7	RST 2
01	LXI B,D16	2C	INR L	57	MOV D,A	82	ADD D	AD	XRA L	D8	RC
02	STAX B	2D	DCR L	58	MOV E,B	83	ADD E	AE	XRA M	D9	-
03	INX B	2E	MVI L,D8	59	MOV E,C	84	ADD H	AF	XRA A	DA	JC Adr
04	INR B	2F	CMA	5A	MOV E,D	85	ADD L	B0	ORA B	DB	IN D8
05	DCR B	30	SIM	5B	MOV E,E	86	ADD M	B1	ORA C	DC	CC Adr
06	MVI B,D8	31	LXI SPD16	5C	MOV E,H	87	ADD A	B2	ORA D	DD	-
07	RLC	32	STA Adr	5D	MOV E,L	88	ADC B	B3	ORA E	DE	SBI D8
08	-	33	INX SP	5E	MOV E,M	89	ADC C	B4	ORA H	DF	RST 3
09	DAD B	34	INR M	5F	MOV E,A	8A	ADC D	B5	ORA L	E0	RPO
0A	LDAX B	35	DCR M	60	MOV H,B	8B	ADC E	B6	ORA M	E1	POP H
0B	DCX B	36	MVI M,D8	61	MOV H,C	8C	ADC H	B7	ORA A	E2	JPO Adr
0C	INR C	37	STC	62	MOV H,D	8D	ADC L	B8	CMP B	E3	XTHL
0D	DCR C	38	---	63	MOV H,E	8E	ADC M	B9	CMP C	E4	CPO Adr
0E	MVI C,D8	39	DAD SP	64	MOV H,H	8F	ADC A	BA	CMP D	E5	PUSH H
0F	RRC	3A	LDA Adr	65	MOV H,L	90	SUB B	BB	CMP E	E6	ANI D8
10	---	3B	DCX SP	66	MOV H,M	91	SUB C	BC	CMP H	E7	RST 4
11	LXI D,D16	3C	INR A	67	MOV H,A	92	SUB D	BD	CMP L	E8	RPE
12	STAX D	3D	DCR A	68	MOV L,B	93	SUB E	BE	CMP M	E9	PCHL
13	INX D	3E	MVI A,D8	69	MOV L,C	94	SUB H	BF	CMP A	EA	JPE Adr
14	INR D	3F	CMC	6A	MOV L,D	95	SUB L	C0	RNZ	EB	XCHG
15	DCR D	40	MOV B,B	6B	MOV L,E	96	SUB M	C1	POP B	EC	CPE Adr
16	MVI D,D8	41	MOV B,C	6C	MOV L,H	97	SUB A	C2	JNZ Adr	ED	---
17	RAL	42	MOV B,D	6D	MOV L,L	98	SBB B	C3	JMP Adr	EE	ERI D8
18	---	43	MOV B,E	6E	MOV L,M	99	SBB C	C4	CNZ Adr	EF	RST 5
19	DAD D	44	MOV B,H	6F	MOV L,A	9A	SBB D	C5	PUSH B	F0	RP
1A	LDAX D	45	MOV B,L	70	MOV M,B	9B	SBB E	C6	ADI D8	F1	POP PSW
1B	DCX D	46	MOV B,M	71	MOV M,C	9C	SBB H	C7	RST 0	F2	JP Adr
1C	INR E	47	MOV B,A	72	MOV M,D	9D	SBB L	C8	RZ	F3	DI
1D	DCR E	48	MOV C,B	73	MOV M,E	9E	SBB M	C9	RET Adr	F4	CP Adr
1E	MVI E,D8	49	MOV C,C	74	MOV M,H	9F	SBB A	CA	JZ	F5	PUSH PSW
1F	RAR	4A	MOV C,D	75	MOV M,L	A0	ANA B	CB	---	F6	ORI D8
20	RIM	4B	MOV C,E	76	HLT	A1	ANA C	CC	CZ Adr	F7	RST 6
21	LXI H,D16	4C	MOV C,H	77	MOV M,A	A2	ANA D	CD	CALL Adr	F8	RM
22	SHLD Adr	4D	MOV C,L	78	MOV A,B	A3	ANA E	CE	ACI D8	F9	SPHL
23	INX H	4E	MOV C,M	79	MOV A,C	A4	ANA H	CF	RST 1	FA	JM Adr
24	INR H	4F	MOV C,A	7A	MOV A,D	A5	ANA L	D0	RNC	FB	EI
25	DCR H	50	MOV D,B	7B	MOV A,E	A6	ANA M	D1	POP D	FC	CM Adr
26	MVI H,D8	51	MOV D,C	7C	MOV A,H	A7	ANA A	D2	JNC Adr	FD	---
27	DAA	52	MOV D,D	7D	MOV A,L	A8	XRA B	D3	OUT D8	FE	CPI D8
28	---	53	MOV D,E	7E	MOV A,M	A9	XRA C	D4	CNC Adr	FF	RST 7
29	DAD H	54	MOV D,H	7F	MOV A,A	AA	XRA D	D5	PUSH D		
2A	LHLD Adr	55	MOV D,L	80	ADD B	AB	XRA E	D6	SUI D8		

D8 = constant, or logical/arithmetic expression that evaluates to an 8-bit data quantity. D16 = constant, or logical/arithmetic expression that evaluates to a 16 bit data quantity. Adr = 16 bit address.

THIS IS THE LAST PRINTED PAGE.