

2506/202

2507/202

ELECTRONICS AND CONTROL SYSTEMS

June/July 2017

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**DIPLOMA IN AERONAUTICAL ENGINEERING
(AIRFRAMES AND ENGINES OPTION)
(AVIONICS OPTION)**

MODULE II

ELECTRONICS AND CONTROL SYSTEMS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Non-programmable scientific calculator.

This paper consists of EIGHT questions in TWO sections; A and B.

Answer THREE questions from section A and TWO questions from section B.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 7 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

SECTION A: ELECTRONICS

Answer **THREE** questions from this section.

1. (a) Perform the following conversions:

(i) $(1101.11)_2$ into decimal; ✓

(ii) $(47C30.19)_{HEX}$ into binary. ✓

(7 marks)

(b) Figure 1 shows a logic circuit diagram. Derive the Boolean expression for the output.

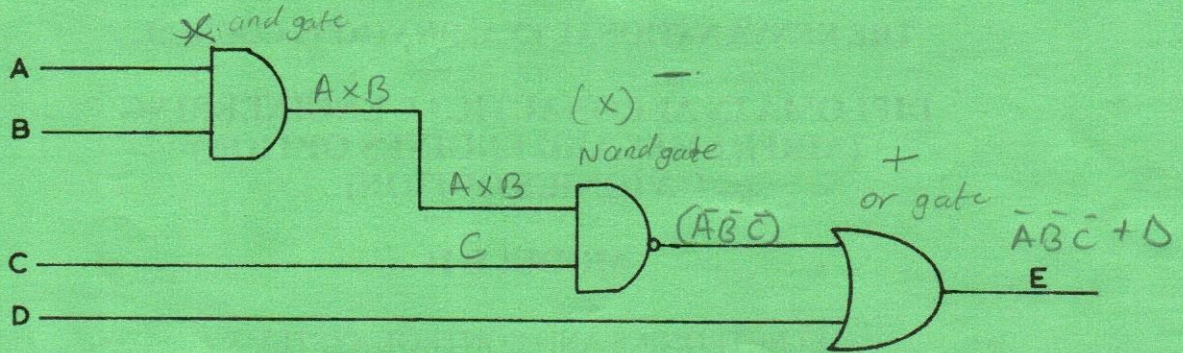


Fig. 1

$$\underline{\underline{(\bar{A}\bar{B}\bar{C}) + D}}$$

(3 marks)

(c) Prove the following Boolean identity:

$$A + \bar{A}B = A + B$$

(4 marks)

(d) With the aid of a circuit diagram, explain the operation of an RTL logic circuit.

(6 marks)

2. (a) State the essential conditions for maintaining oscillations in an oscillator. (2 marks)

(b) A quartz crystal resonating at 450 kHz has an equivalent inductance of 4.2 H, an equivalent capacitance of 0.0297 pF, connected in series with a resistance of 60Ω . Determine the:

(i) equivalent impedance in ohms;

(ii) Q factor.

(8 marks)

(c) With the aid of a two transistor analogy of the silicon controlled rectifier, explain the regeneration of current in the device.

(6 marks)

(d) A tunnel diode has the following data:

$$I_p = 2 \text{ mA at } V_p = 60 \text{ mV.}$$

$$I_v = 0.15 \text{ mA at } V_v = 350 \text{ mV.}$$

Determine the resistance of the tunnel diode.

(4 marks)

3. (a) With the aid of energy band diagrams, explain conductivity in each of the following:

- (i) conductor;
- (ii) insulator;
- (iii) semiconductor.

(9 marks)

(b) (i) Define an intrinsic semiconductor.

*pure
doped semiconductor*

(ii) With the aid of a lattice diagram, explain the formation of an N-type semiconductor.

(7 mark)

(c) Figure 2 shows a fixed bias silicon amplifier circuit diagram. Determine the DC voltages at point:

- (i) TP_1 ;
- (ii) TP_2 .

(4 marks)

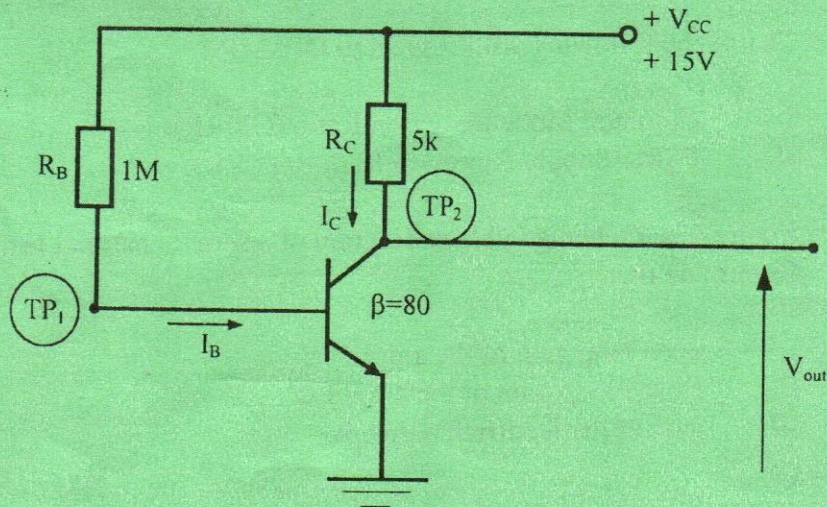


Fig. 2

4. (a) With the aid of a diagram, describe the construction and operation of N-junction Field Effect transistor.

(6 marks)

(b) State **three** advantages of FETs over Bipolar transistors.

(3 marks)

2506/202

2507/202

June/July 2017

(c) Figure 3 shows a circuit diagram of a voltage stabilizer. The zener diode used in the regulator circuit has a voltage V_{in} that can be varied from 20 V to 30 V. Determine the:

- (i) minimum and maximum currents in the zener;
- (ii) the minimum and maximum power dissipated in the diode;
- (iii) maximum rated power dissipation that R_s should have.

Assume the zener diode remains in breakdown.

(11 marks)

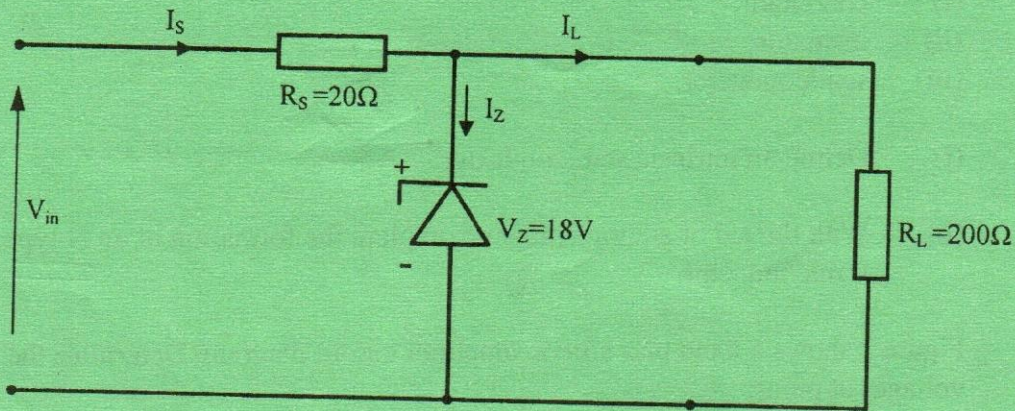


Fig. 3

5. (a) List **four** characteristics of an ideal operational Amplifier (OPAMP). (4 marks)

(b) (i) Define the following with respect to OPAMPs:

- I. Common Mode Rejection Ratio (CMRR);
- II. Power Supply Rejection Ration (PSRR).

(4 marks)

(ii) Figure 4 is a schematic block diagram of a series - parallel feedback amplifier. Determine the:

- I. open loop gain of the amplifier;
- II. closed loop gain of the amplifier;
- III. gain of the feedback network.

(6 marks)

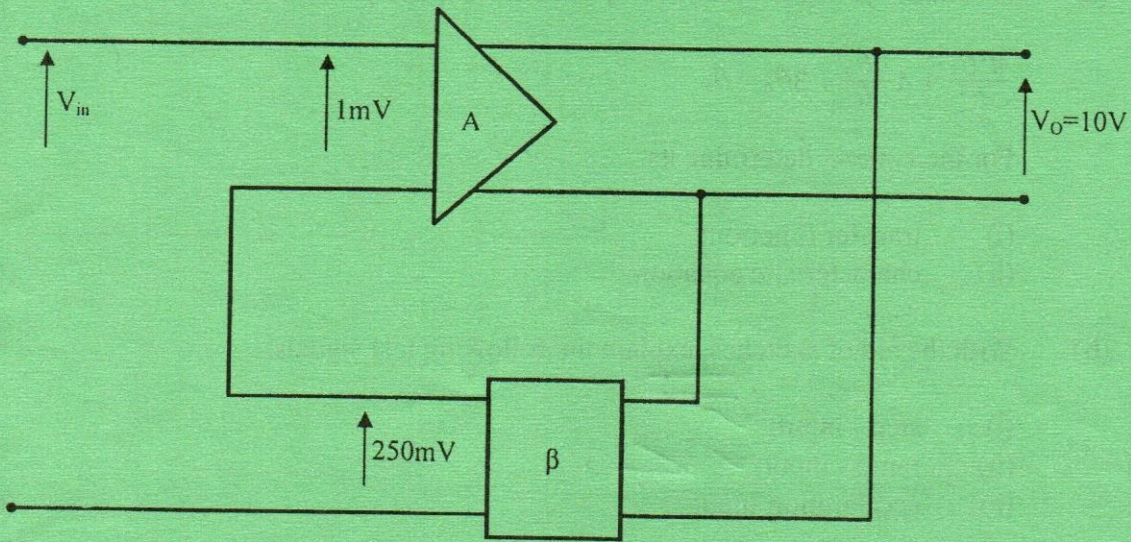


Fig. 4

- (c) With the aid of a circuit diagram, explain the operation of a controlled full wave rectifier. (6 marks)

SECTION B: ENGINEERING CONTROL SYSTEMS

Answer **TWO** questions from this section.

6. (a) With the aid of block diagrams, explain each of the following control systems:
- open loop;
 - closed loop. (8 marks)
- (b) Highlight **four** merits of using closed loop control systems. (4 marks)
- (c) (i) Define 'Transfer Function' as used in control systems. *d/p*
1/p.
- (ii) Explain the following as applied in control systems:
- signal flow graphs;
 - forward path;
 - loop gain. (8 marks)

7. (a) A control system is described by the differential equation:

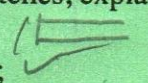

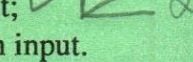
$$\frac{d^2\theta_0}{dt^2} + 4\frac{d\theta_0}{dt} + 3\theta_0 = \theta_i$$

For the system, determine its:

- (i) transfer function; ✓
- (ii) characteristic equation. ✓

(6 marks)

(b) With the aid of sketches, explain the following test signals:

- (i) step - input; ✓ 
- (ii) ramp - input; ✓ 
- (iii) acceleration input. ✓ 

(6 marks)

(c) (i) Define the following as applied to control systems in system response:

- I. settling time; ✓
- II. overshoot. ✓

(ii) The characteristic equation of a second order system is given by:

$$S^2 + 0.6S + 9 = 0$$

Determine the:

- I. natural frequency; ω_n
- II. damped natural frequency. $\omega_d = 1$

(8 marks)

$$\frac{d^2\theta_0}{dt^2} + 4\frac{d\theta_0}{dt} + 3\theta_0 = \theta_i$$


$$\frac{d}{dt} = s$$

$$s^2\theta_0 + 4s\theta_0 + 3\theta_0 = \theta_i$$

$$\theta_0 [s^2 + 4s + 3] = \theta_i$$

$$\frac{\theta_0}{\theta_i} = \frac{1}{s^2 + 4s + 3}$$

$$\text{The eqn} = s^2 + 4s + 3$$

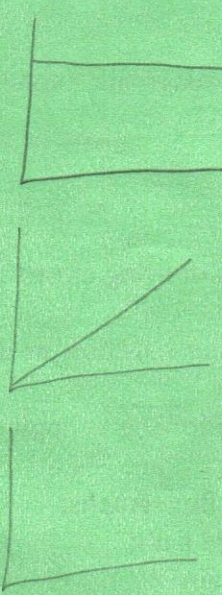

8. (a) Figure 5 shows a circuit diagram of a summing amplifier computing different level voltages. Determine the output, e_o .

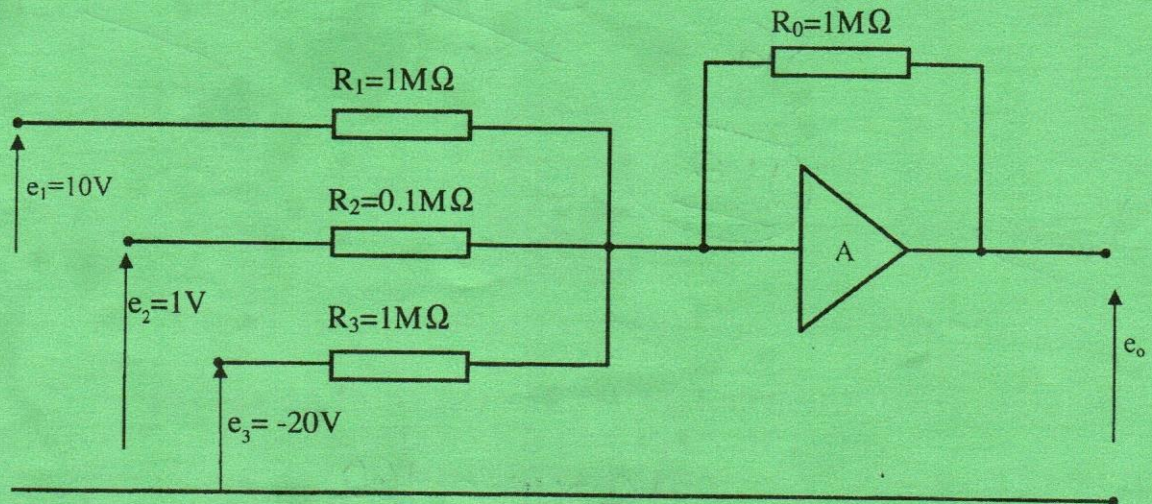


Fig. 5

(4 marks)

- (b) A control system is represented by the equation:

$$\tau \frac{dx}{dt} + x = y;$$

Draw a computer simulation diagram for the system.

(6 marks)

- (c) (i) Define the following with respect to control system stability:

I. gain margin (G_m)

II. phase margin (ϕP_m).

(4 marks)

- (ii) With the aid of a diagram, describe the construction of a synchro transmitter - receiver system.

(6 marks)

THIS IS THE LAST PRINTED PAGE.