

2207/302

TELECOMMUNICATION PRINCIPLES

Oct./Nov. 2019

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**DIPLOMA IN AERONAUTICAL ENGINEERING (AVIONICS)  
(COMMUNICATION AND NAVIGATION OPTION)**

TELECOMMUNICATION PRINCIPLES

3 hours

**INSTRUCTIONS TO CANDIDATES**

*You should have the following for this examination:*

*Answer booklet;*

*Mathematical tables/Non-programmable scientific calculator;*

*Drawing instruments.*

*Answer FIVE of the EIGHT questions in the answer booklet provided.*

*All questions carry equal marks.*

*Maximum marks for each part of a question are as indicated.*

*Candidates should answer the questions in English.*

**This paper consists of 8 printed pages.**

**Candidates should check the question paper to ascertain that  
all the pages are printed as indicated and that no questions are missing.**

$$V_o = \frac{1}{1 + \beta V}$$

1. (a) Define each of the following with respect to tuned circuits:

- (i) resonant frequency;
- (ii) selectivity.

(2 marks)

(b) A class-A r.f. amplifier has a load circuit consisting of an inductor of  $100 \mu\text{H}$  in parallel with a lossless capacitor of  $200 \text{ pF}$ . The effective Q-factor of the inductor is 56 and the output voltage at resonance is 10 V. Determine the:

- (i) resonant frequency;
- (ii) bandwidth;
- (iii) lower cutoff frequency;
- (iv) upper cutoff frequency;
- (v) output voltage at the cutoff frequencies.

(10 marks)

(c) (i) State **two** effects of applying negative feedback to an amplifier.

(ii) A voltage amplifier has a gain of 47 dB without negative feedback. Determine the:

- (I) voltage gain without feedback as a ratio;
- (II) voltage gain when 25% of the output voltage is fed back as negative feedback;
- (III) reduction in harmonic distortion when negative feedback is applied.

(8 marks)

2. (a) (i) State **three** applications of silicon controlled rectifiers.

(ii) Sketch the characteristic curve of a unijunction transistor and explain its shape.

(8 marks)

(b) With the aid of a circuit diagram, describe the operation of a synchro system for detecting angular misalignment between two shafts.

(6 marks)

(c) A thermocouple is made up of tellurium having sensitivity of  $500 \mu\text{V}/^\circ\text{C}$  and bismuth having a sensitivity of  $-72 \mu\text{V}/^\circ\text{C}$ . The measuring junction is subjected to an increase in temperature of  $150^\circ\text{C}$ . The total circuit resistance is  $320 \Omega$ . Determine the:

- (i) sensitivity of the thermocouple;
- (ii) maximum output voltage;
- (iii) maximum output current.

(6 marks)

3. (a) (i) Define each of the following with respect to amplitude modulation (AM):

- (I) side frequency;
- (II) modulation envelope.

(ii) Figure 1 shows a circuit diagram of an AM modulator. Describe its operation. (6 marks)

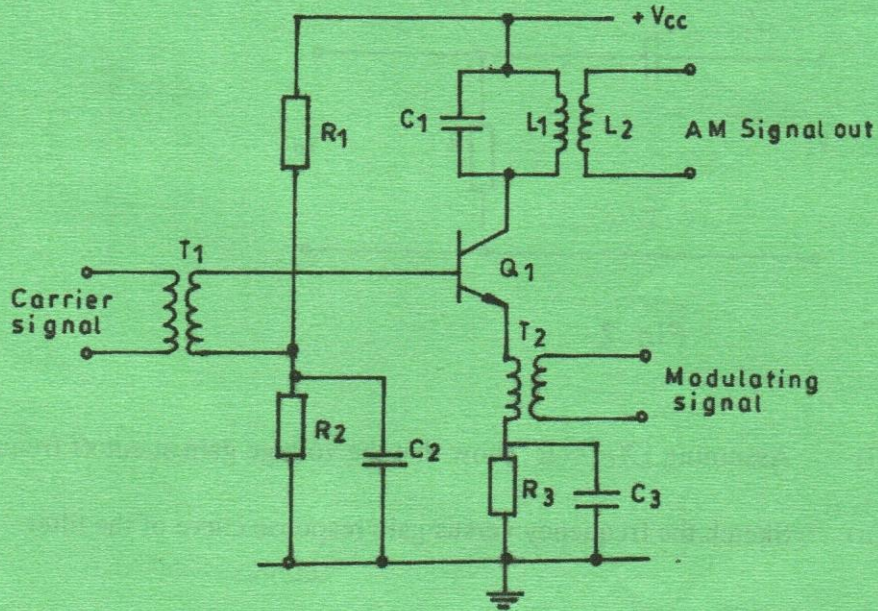


Fig. 1

(b) A 10V, 1MHz carrier signal is amplitude modulated by a sinusoidal signal. The amplitude of the lower side frequency is 4 V at 980 kHz. Determine the:

- (i) modulation index;
- (ii) amplitude of the modulating signal;
- (iii) frequency of the modulating signal;
- (iv) bandwidth required to transmit the modulated signal.

(8 marks)

(c) (i) Distinguish between pulse width modulation and pulse position modulation.

(ii) A pulse code modulation system has a bit rate of 72 kilobytes per second at a sampling frequency of 8 kHz. If each sample is accompanied by one synchronization bit, determine the:

- (I) quantization level, in bits;
- (II) bandwidth.

(6 marks)

4. (a) (i) State **two** factors that determine the natural frequency of a piezoelectric crystal.
- (ii) With the aid of a labelled block diagram, describe the operation of a sinusoidal oscillator.

(8 marks)

- (b) Figure 2 shows a circuit diagram of an R-C filter.

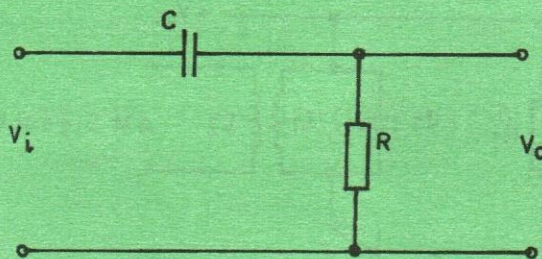


Fig. 2

- (i) Assuming  $|X_C| = R$ , show that the voltage gain at cutoff frequency is  $-3$  dB.
- (ii) Sketch the frequency versus gain response curve of the filter.

(6 marks)

- (c) The tuned circuit of an oscillator consists of a  $22$  pF capacitor in parallel with a  $50$   $\mu$ H,  $12$   $\Omega$  inductor. For the tuned circuit, determine the:

- (i) resonant frequency;
- (ii) Q-factor;
- (iii) dynamic impedance.

(6 marks)

5. (a) (i) Define each of the following with respect to radio wave propagation:

- (I) fading;
- (II) ionosphere.

- (ii) With the aid of a ray diagram, explain radio horizon for space waves.

(6 marks)

- (b) Figure 3 shows a circuit diagram illustrating a generator, having an impedance  $Z_O$ , connected to the input terminals of a transmission line which is terminated in an impedance  $Z_R$ . Assuming the  $Z_O$  is not equal to  $Z_R$ , show that the reflection coefficient,  $\rho$ , is given by the expression

$$\rho = \frac{Z_O - Z_R}{Z_O + Z_R}$$

(8 marks)

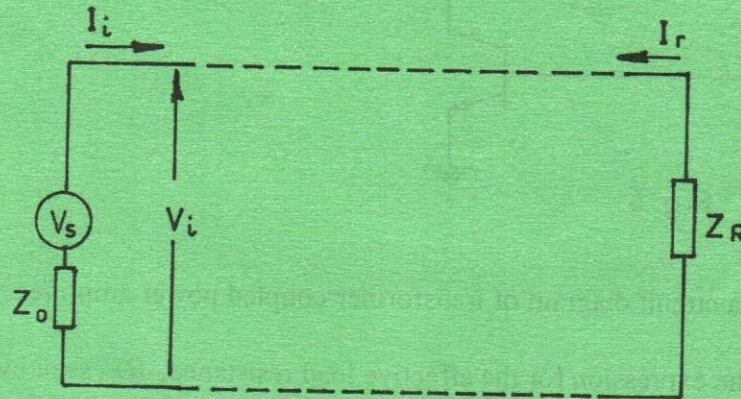


Fig. 3

- (c) A transmission line has inductance of 6 mH/km and capacitance of 0.056  $\mu$ F/km. The frequency of operation is 1.5 kHz. Determine the:

- (i) phase delay;
- (ii) wavelength;
- (iii) velocity of propagation.

(6 marks)

6. (a) Figure 4 shows a circuit diagram of a common-emitter amplifier in which the values of  $h_{re}$  and  $h_{oe}$  of the transistor are negligible.

- (i) Draw the h-parameter equivalent circuit.
- (ii) Taking  $h_{fe} = 50$  and  $h_{ie} = 1 \text{ k}\Omega$ , determine the:

- (I) voltage gain;
- (II) current gain;
- (III) input impedance;
- (iv) output impedance.

(12 marks)

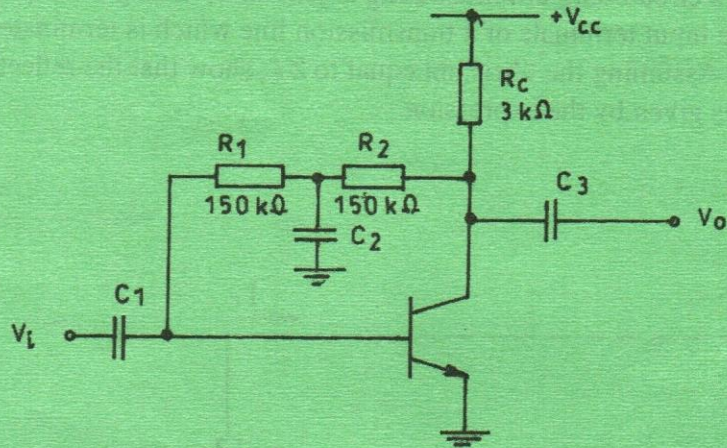


Fig. 4

(b) Figure 5 shows a circuit diagram of transformer-coupled power amplifier.

- (i) Obtain the expression for the effective load resistance,  $R'_L$ , seen by the collector circuit.
- (ii) Determine the transformer turns ratio required to match a  $16 \Omega$  load to the amplifier so that  $R'_L = 10 \text{ k}\Omega$ .

(8 marks)

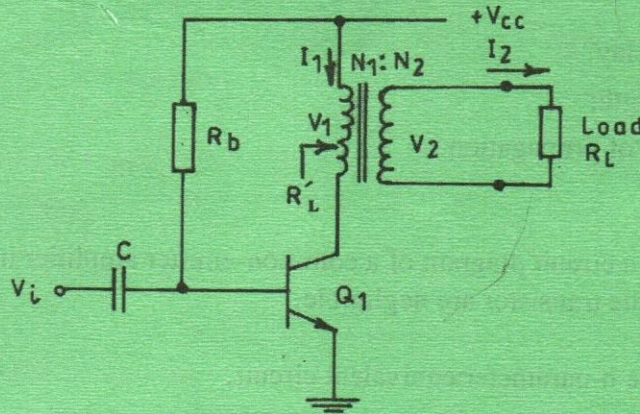


Fig. 5

7. (a) (i) State **two** services that use narrowband FM.
- (ii) With the aid of a circuit diagram, describe the operation of a varactor diode FM modulator.

(8 marks)

(b) Figure 6 shows a circuit diagram of a balanced slope FM demodulator.

- (I) Describe its operation.  
 (II) Sketch its response curve.

(6 marks)

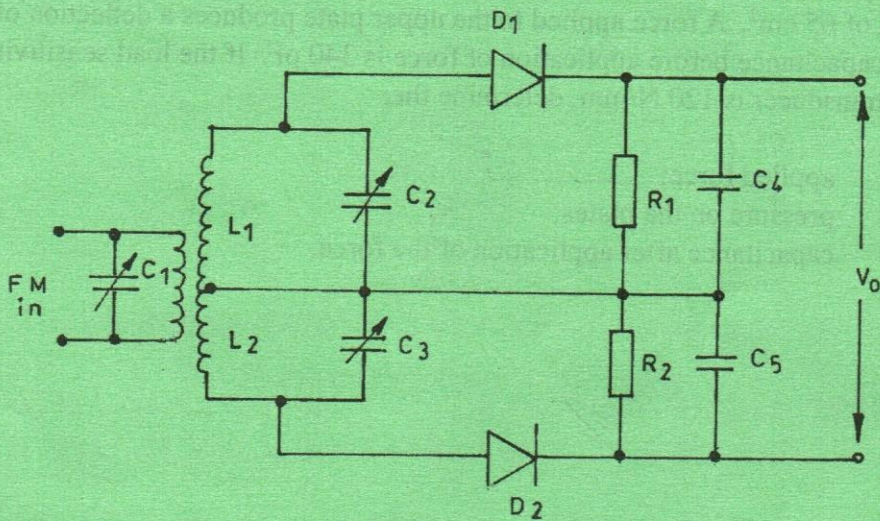


Fig. 6

(c) A 3V, 600 Hz audio modulating signal produces a frequency deviation of 5 kHz in an FM system. If the amplitude of the audio signal is increased to 8 V, determine the:

- (i) sensitivity of the system;  
 (ii) new frequency deviation;  
 (iii) new modulation index.

(6 marks)

8. (a) State:

- (i) two areas of application of wideband amplifiers;  
 (ii) two effects of cascading tuned amplifiers.

(4 marks)

(b) Table 1 shows various frequency bands and their classifications. Complete the table.

(4 marks)

Frequency	Classification
	Very low frequency
300 kHz - 3,000 kHz	
	Very high frequency
3 GHz - 30 GHz	

- (c) With the aid of a labelled block diagram, describe the filter method of generating a single sideband signal. (6 marks)
- (b) A capacitive transducer uses two plates separated by an air gap of 3 mm and effective area of 65 cm<sup>2</sup>. A force applied to the upper plate produces a deflection of 0.8 mm and the capacitance before application of force is 340 pF. If the load sensitivity of the transducer is 120 N/mm, determine the:
- applied force;
  - pressure on the plates;
  - capacitance after application of the force.
- (6 marks)

*Stefan*

**THIS IS THE LAST PRINTED PAGE.**

*Answer*  
*Answer*  
*Answer*

*Answer*

*Answer*

*5 x 6000*  
*30000*

*10000*  
*240,000*

*Answer*

*1000*  
*x 30*  
*30,000*  
*360,000*  
*x 6*  
*300*

*3000*  
*x 600*

*1.5 k*

*Answer*

*Answer*