

2507/207

ELECTRIC CIRCUIT ANALYSIS

Oct./Nov. 2019

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**DIPLOMA IN AERONAUTICAL ENGINEERING
(AVIONICS OPTION)**

MODULE II

ELECTRIC CIRCUIT ANALYSIS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Non-programmable scientific calculator;

Drawing instruments.

Answer any FIVE of the EIGHT questions in the answer booklet provided.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 7 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

1. (a) (i) Define a 'Two-Port Network'.
- (ii) List **one** example of each of the following types of two-port network:
- (I) Active network;
- (II) Passive network. (4 marks)

- (b) (i) Transmission -line parameters in a two -port network are given as

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

Express the equations in matrix form.

- (ii) Using the equations in b(i) determine the:

- (I) short circuit transfer admittance;
- (II) open circuit transfer impedance. (6 marks)

- (c) (i) Explain the following terms:

- (I) complex wave;
- (II) harmonics.

- (ii) A complex wave of rms value of 240 V has 22 % third harmonic and 5% fifth harmonic contents.

Determine the rms value of the:

- (I) fundamental waveform;
- (II) 3rd and 5th harmonic contents. (10 marks)

2. (a) (i) With aid of a labelled phasor diagram, derive the relationship between the line voltage (V_L) and phase voltage (V_p) in a three phase star connected balanced system.
- (ii) Write an expression for electric power delivered in the system. (9 marks)

- (b) Draw the two-wattmeter method of power measurement in a three phase three wire star connected distribution system. (4 marks)

- (c) The input power to a three phase load is measured by a two wattmeter method and the readings obtained are 6.8 kW and -3.6 kW. The line voltage is 415 V.

Determine the:

- (i) total active power;
- (ii) power factor. (7 marks)

3. (a) (i) Explain why the stator core of a three phase induction motor is made of sheet steel.
- (ii) Draw a labelled construction diagram of a wound rotor of a three phase induction motor.
- (iii) State **one** advantage of the of the rotor in (ii) over the squirrel cage rotor. (7 marks)
- (b) A three phase, 6 pole 50 Hz induction motor has ship of 1% at no-load and a slip of 3% at full-load.
Determine the:
- (i) synchronous speed;
- (ii) no-load speed;
- (iii) full-load speed;
- (iv) frequency of rotor current at standstill. (8 marks)
- (c) (i) Illustrate each of the following methods of transformer winding connections:
- (I) Delta-Delta;
- (II) Delta-Star.
- (ii) List **one** method of transformer cooling. (5 marks)
4. (a) Draw a labelled construction diagram of a d.c machine. (4 marks)
- (b) (i) Illustrate each of the following types of armature windings:
- (I) lap winding;
- (II) wave winding.
- (ii) A 8-pole lap wound d.c. machine has 960 conductors and a flux of 40 mWb per pole. If the machine rotates at 400 rpm, determine the emf induced. (7 marks)
- (c) (i) Explain the need for starters in d.c. motors.
- (ii) Figure 1 shows a d.c motor face-plate starter:
- (I) Name the parts labelled 1 – 5.
- (II) Explain the functions of the parts labelled 2 and 3 respectively. (9 marks)

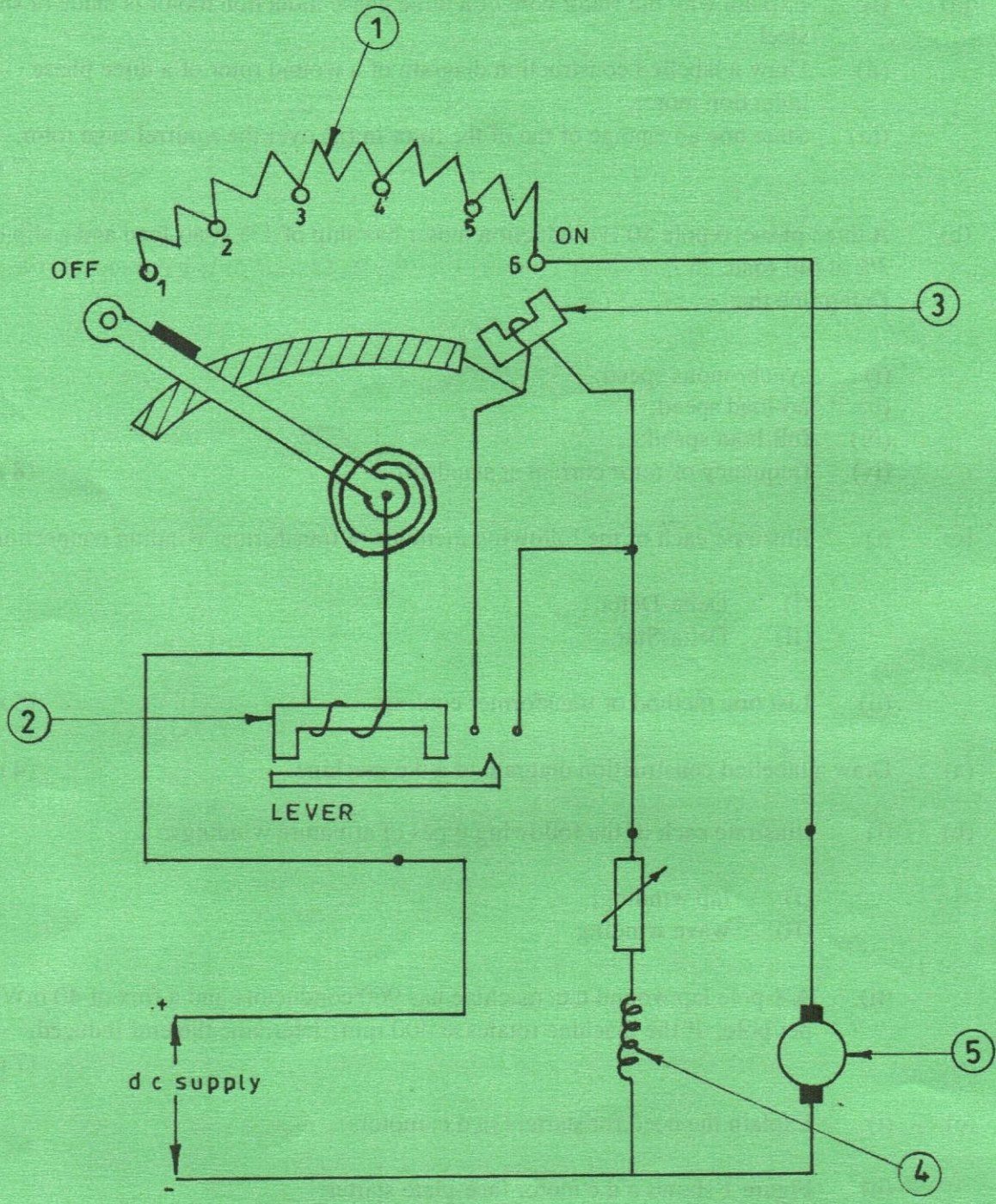


Fig. 1

5. (a) Define the following terms with reference to transients:
- transient period;
 - steady state period. (4 marks)
- (b) With the aid of a circuit diagram, explain the growth of current in a d.c. R - L circuit. (6 marks)
- (c) A $10 \mu\text{F}$ capacitor is connected in series with a 50Ω resistor to a d.c supply of E volts. After 0.7 seconds, the voltage across the resistor is 20 V. Determine the value of:
- supply voltage E ;
 - charging current 1.4 seconds after power supply is switched on. (6 marks)
- (d) Figure 2 shows a capacitor discharge circuit, show that $V_c + RC \frac{dV_c}{dt} = 0$ where V_c is capacitor voltage. (4 marks)

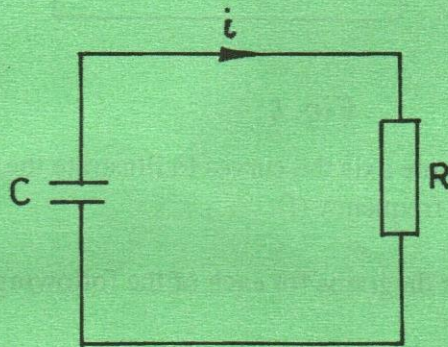


Fig. 2

6. (a) State the maximum power transfer theorem. (2 marks)
- (b) Figure 3 shows a bridge circuit with $R_a = 20 \Omega$, $R_b = 30 \Omega$, $R_c = 50 \Omega$, $R_d = 5 \Omega$ and $R_e = 24 \Omega$.
- Transform the delta formed by the resistances R_a , R_b and R_c into star equivalent.
 - Draw the equivalent circuit diagram in b(i) and determine the current supplied by the battery. (14 marks)

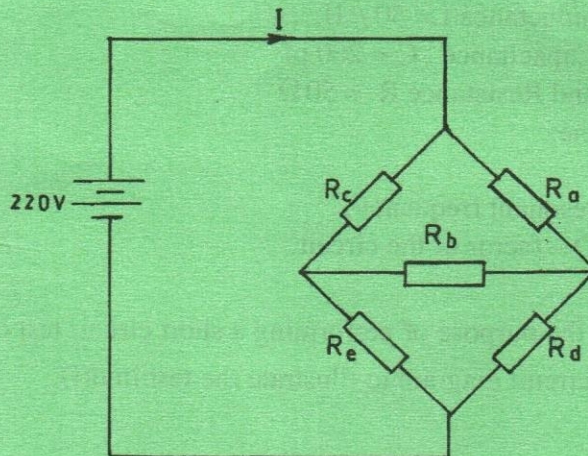


Fig. 3

- (c) (i) Figure 4 shows R – L – C series a.c. circuit. Write the expression for the circuit current I.

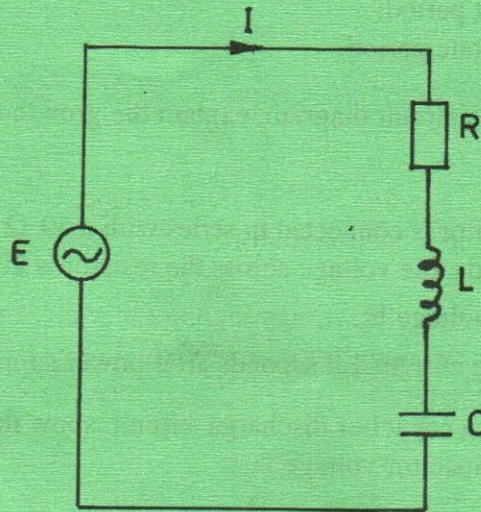


Fig. 4

- (ii) Sketch on the same axis the curves to illustrate the variation of the reactances X_L and X_C with frequency (f). (4 marks)

7. (a) Draw equivalent circuit diagrams for each of the following types of d.c. machines:

- (i) long compounded motor;
 (ii) separately excited d.c. generator. (4 marks)

- (b) Sketch, on the same axis the torque versus armature current characteristic curves for:

- (i) d.c. shunt motor;
 (ii) d.c. series motor. (4 marks)

- (c) (i) Define 'Q-factor as applied in ac series R–L–C circuits.

- (ii) An a.c. series R–L–C circuit has
 inductance $L = 50 \mu\text{H}$,
 Capacitance, $C = 200 \text{ pF}$
 and Resistance $R = 50 \Omega$

Determine;

- (I) resonant frequency;
 (II) Q – factor of the circuit. (7 marks)

- (d) (i) Explain the purpose of performing a short circuit test on a transformer.
 (ii) Draw a circuit diagram to illustrate the test in d(i). (5 marks)

8. (a) Define each of the following terms as use in d.c. machines:
- (i) commutation;
 - (ii) armature reaction. (4 marks)
- (b) Sketch the open circuit characteristic curve for a d.c. shunt generator. (3 marks)
- (c) With the aid of a labelled cross-sectional diagram, explain the operation of a single phase shaded pole induction motor. (8 marks)
- (d) (i) Define synchronization as applied in synchronous machines.
(ii) State **three** conditions to be satisfied before a three phase synchronous motor is connected to an existing three phase supply. (5 marks)

THIS IS THE LAST PRINTED PAGE.