

2506/202

2507/202

**ELECTRONICS AND CONTROL  
SYSTEMS**

**June/July 2019**

**Time: 3 hours**



**THE KENYA NATIONAL EXAMINATIONS COUNCIL**

**DIPLOMA IN AERONAUTICAL ENGINEERING  
(AIRFRAMES AND ENGINES OPTION)  
(AVIONICS OPTION)**

**MODULE II**

**ELECTRONICS AND CONTROL SYSTEMS**

**3 hours**

**INSTRUCTIONS TO CANDIDATES**

*This paper consists of **EIGHT** questions in **TWO** sections, **A** and **B**.*

*Answer **THREE** questions from section **A** and **TWO** questions from section **B** in the answer booklet provided.*

*All questions carry equal marks.*

*Maximum marks for each part of a question are as indicated.*

*Candidates should answer the questions in English.*

**This paper consists of 7 printed pages.**

**Candidates should check the question paper to ascertain that  
all the pages are printed as indicated and that no questions are missing.**



## SECTION A: ELECTRONICS TECHNOLOGY

Answer **THREE** questions from this section.

1. (a) Distinguish between forward biasing and reverse biasing with respect to semi conductor diodes. (2 marks)
- (b) (i) State **two** advantages of full-wave bridge rectifiers over centre-tapped full-wave rectifiers.
- (ii) With the aid of a diagram, describe the operation of a centre-tapped full-wave rectifier. (10 marks)
- (c) A P-N junction diode having internal resistance ( $r$ ) of  $20\ \Omega$  is used for half-wave rectification. The applied voltage,  $V = 50 \sin \omega t$  and load resistance  $R_L = 800\ \Omega$ . Determine the:
- (i) maximum current ( $I_m$ );
- (ii) direct current  $I_{dc}$ ;
- (iii) root mean square current ( $I_{rms}$ );
- (iv) d.c output voltage. (8 marks)
2. (a) List **two** applications of Light Emitting Diodes (LEDs). (2 marks)
- (b) Draw the symbols of the following devices:
- (i) silicon controlled rectifier;
- (ii) LED;
- (iii) varactor diode. (6 marks)
- (c) State **two** classes of power amplifiers with respect to their mode of operation. (2 marks)
- (d) An amplifier has an open circuit voltage gain of 1,000, an output resistance of  $15\ \Omega$  and input resistance of  $7\ \text{K}\Omega$ . It is supplied from a signal source of e.m.f  $10\ \text{mV}$  with internal resistance of  $3\ \text{K}\Omega$ . The amplifier feeds a load of  $35\ \Omega$ .
- (i) sketch the equivalent circuit for the amplifier;
- (ii) Determine the:
- I. magnitude of the input voltage;
- II. magnitude of the output voltage. (10 marks)



3. (a) State **three** merits of sinusoidal oscillators. (3 marks)
- (b) With the aid of a diagram, describe the construction of a colpitt's oscillator. (7 marks)
- (c) State **three** merits of common emitter configuration with respect to bipolar junction transistors (BJTs). (3 marks)
- (d) Figure 1 shows a PNP transistor. The zero signal base current is  $20 \mu A$  and  $\beta = 50$ .
- (i) Determine the quiescent (Q) point;
- (ii) draw the load line. (7 marks)

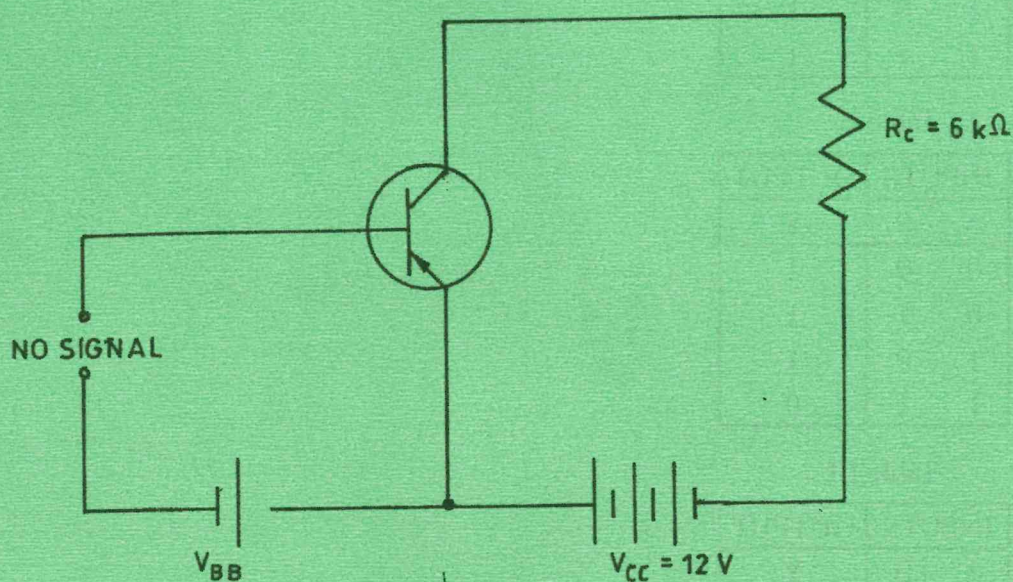


Fig.1

4. (a) Define the following with respect to memories:
- (i) access time;
- (ii) memory cell. (2 marks)



(b) Tables I, II and III show truth tables for different logic gates:

(i) identify the logic gates;

(ii) draw the symbols in (i);

(iii) write the Boolean expressions for the gates in (i).

(9 marks)

Table I

INPUTS		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Table II

INPUTS		OUTPUT
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Table III

INPUTS		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

(c) With the aid of a logic circuit diagram, describe the operation of a clocked J - K flip-flop.

(9 marks)

5. (a) Convert the following:

(i)  $27.25_{10}$  into binary;

(ii)  $64.075_{10}$  into octal;

(iii)  $4AF.9_{16}$  into octal.

(9 marks)



- (b) Write the Boolean equivalence of the following:
- (i)  $A.1 =$ ;
  - (ii)  $A + 1 =$ ;
  - (iii)  $A + AB =$  (3 marks)
- (c) Add  $37_{10}$  and  $49_{10}$  in excess 3 code. (4 marks)
- (d) Draw a logic circuit of a 2 to 4 decoder. (4 marks)

## SECTION B: CONTROL SYSTEMS

*Answer TWO questions from this section*

6. (a) Define the following:
- (i) settling time;
  - (ii) delay time;
  - (iii) peak time. (3 marks)
- (b) Draw a 2<sup>nd</sup> order systems response curve showing the following:
- (i) overshoot;
  - (ii) rise time;
  - (iii) peak time. (7 marks)
- (c) A unity negative feedback control system has a forward transfer function:
- $$G(s) = \frac{K}{(S + a_1)(S + a_2)}$$
- (i) draw the block diagram of the system;
  - (ii) determine the closed loop transfer function. (6 marks)
- (d) draw a three-input summer operational amplifier circuit. (4 marks)



7. (a) State Routh's stability criterion. (2 marks)

(b) The open loop transfer function of a control system is given by:

$$G(s) = \frac{K}{s(s^2 + s + 1)(s + 4)}$$

The system has a unity feedback. Determine the characteristic equation. (4 marks)

(c) A second order system is describe by the differential equation:

$$3 \frac{d^2 \theta_0}{dt^2} + 6 \frac{d\theta_0}{dt} = 12 E. \text{ Where } E = (\theta_i - \theta_0).$$

Determine the:

(i) undamped natural frequency;

(ii) damping factor;

(iii) percentage overshoot;

(iv) time taken to reach the overshoot. (8 marks)

(d) With the aid of a diagram, describe components of a servo system. (6 marks)

8. (a) State **three** advantages of the bode plots over polar plots. (3 marks)

(b) Figure 2 shows an RLC circuit having a  $150 \, \Omega$  resistance,  $0.06 \, \text{H}$  inductor and a  $67 \, \mu\text{F}$  capacitor.

Determine the:

(i) transfer function;

(ii) resonant frequency. (6 marks)


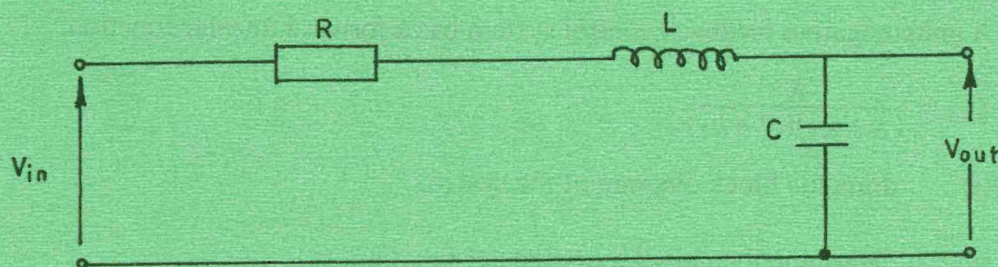


Fig. 2

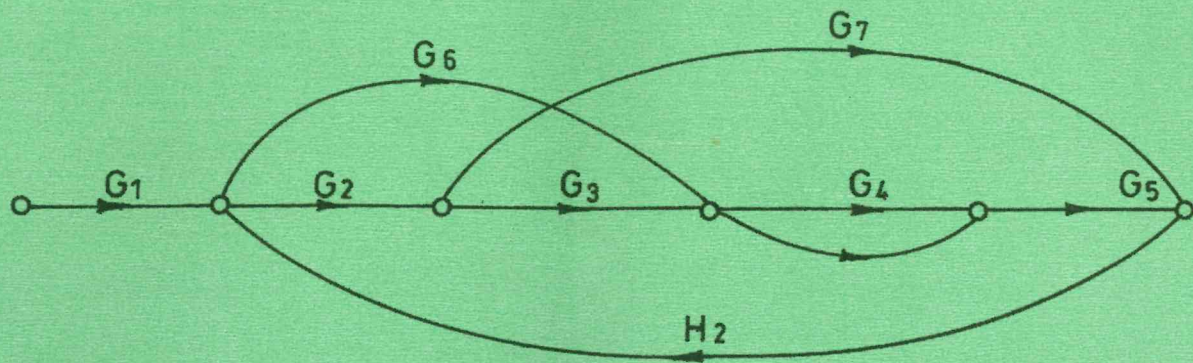

- (c) Figure 3 shows a signal flow graph of a control system. Using Mason's gain formula determine the closed loop transfer function. (8 marks)



$$T.F = \frac{G_1 G_2 G_3 G_4 G_5 + G_1 G_2 G_3 G_4 G_5}{1 - G_6 G_7 - H_2 G_1 G_2 G_3 G_4 G_5}$$

Fig.3

- (d) Highlight **three** characteristics of an ideal operational amplifier (OP - AMP). (3 marks)

**THIS IS THE LAST PRINTED PAGE.**