

2506/202
2507/202
ELECTRONICS AND
CONTROL SYSTEMS
Oct./Nov. 2021
Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL
DIPLOMA IN AERONAUTICAL ENGINEERING
(AIRFRAMES AND ENGINES OPTION)
(AVIONICS OPTION)

MODULE II

ELECTRONICS AND CONTROL SYSTEMS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Mathematical tables/Non-programmable scientific calculator;

Drawing instruments;

Laplace transform tables.

This paper consists EIGHT questions in TWO sections; A and B.

Answer THREE questions from section A and TWO questions from section B in the answer booklet provided.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 8 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

SECTION A: ELECTRONICS

Answer **THREE** questions from this section.

1. (a) Convert the decimal number 3749 into:

- (i) octal;
- (ii) binary;
- (iii) hexadecimal;
- (iv) BCD.

(8 marks)

(b) A Boolean function is defined by

$$f(x_1x_2x_3) = \sum(0,1,3,5)$$

Implement the function using:

- (i) minimal gates;
- (ii) decoder and OR-gate(s);
- (iii) 4-to-1 multiplexer.

(12 marks)

2. (a) (i) Draw an orbital diagram to illustrate the electron arrangement of:



(ii) State **two** elements used to produce N-type semiconductors when added to silicon.

(6 marks)

(b) With the aid of a V-I characteristic curve, explain the operation of a tunnel diode.

(5 marks)

(c) Figure 1 shows a circuit diagram of a common-emitter amplifier.

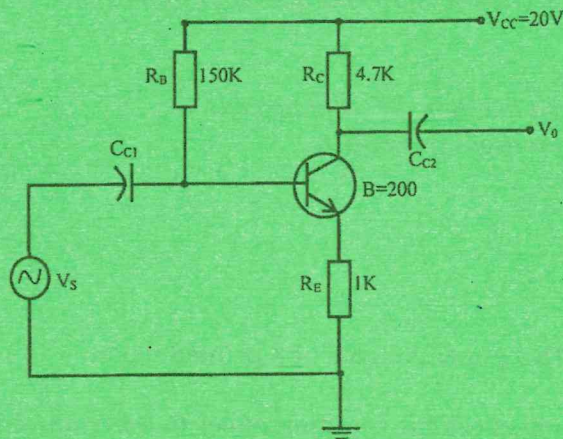


Fig. 1

Determine the values of the:

- (i) input resistance looking directly into the base;
- (ii) input resistance of the stage;
- (iii) voltage gain, in dB.

(9 marks)

3. (a) Distinguish between bistable and astable multi-vibrators. (2 marks)

(b) Figure 2 shows a circuit diagram of an OPamp-based oscillator.

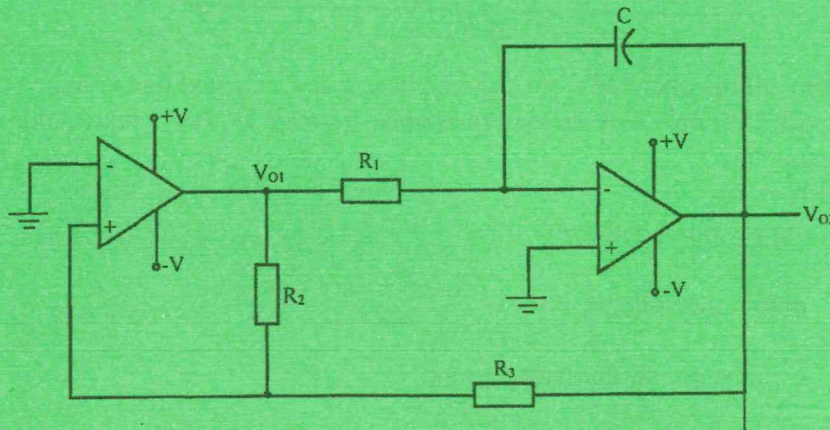


Fig. 2

(i) Draw the waveforms at:

(I) V_{o1} ;

(II) V_{o2} .

(ii) Explain the working of the circuit.

(8 marks)

(c) State **two** advantages of LCD displays over CRT displays.

(2 marks)

- (d) Figure 3 shows a circuit diagram of a three-phase half-wave converter.

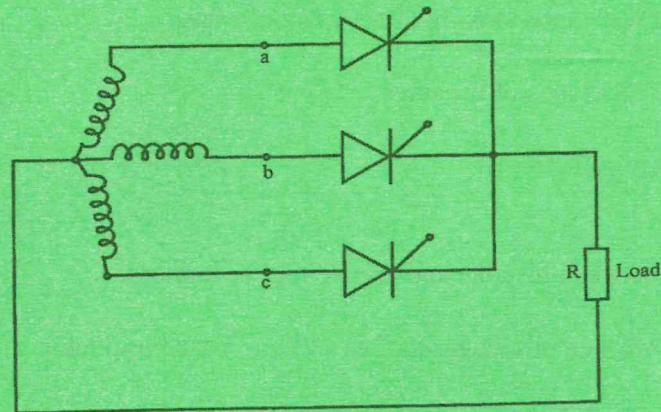


Fig. 3

The converter is operated from a three phase star-connected line voltage of 415 V, 50 Hz supply and the load resistance, $R = 10 \Omega$. For a delay angle of 67° , determine the:

- (i) supply phase voltage;
- (ii) output d.c voltage;
- (iii) average output thyristor current.

(6 marks)

- (e) State **two** merits of three-phase controlled inverters.

(2 marks)

4. (a) (i) With the aid of a schematic block diagram describe the operation of a 4-bit serial adder.

- (ii) State **one** merit and **one** demerit of a carry-look-ahead adder. (8 marks)

- (b) (i) Define each of the following with respect to computer memories:

(I) memory card;

(II) access time.

- (ii) Draw a circuit diagram of a DRAM memory cell and describe its operation.

(8 marks)

- (c) A memory is defined as 512K X 8. Determine for the memory:

- (i) word size;
- (ii) capacity;
- (iii) number of address lines.

(4 marks)

5. (a) Draw the truth table of a JK-flip flop. (3 marks)
- (b) A new clocked X-Y flip flop is defined with two inputs X and Y in addition to the clock input. The flip-flop functions as follows:
- If XY = 00, the flip-flop changes state with each clock pulse;
 - If XY = 01, the flip-flop Q output becomes 1 with the next clock pulse;
 - If XY = 10, the flip-flop state Q becomes 0 with the next clock;
 - If XY = 11, no change of state occurs with the next clock pulse.
- (i) Draw the truth table for the X-Y flip-flop;
- (ii) Write down the excitation table for the X-Y flip-flop;
- (iii) Draw a logic circuit diagram to implement the X-Y flip-flop using JK flip-flop and other gates. (9 marks)
- (c) An asynchronous counter counts from 0 to 13.
- (i) Determine the number of flip-flops required to implement the counter.
- (ii) Draw a logic circuit diagram of the counter, using JK flip-flops. (8 marks)

SECTION B: CONTROL SYSTEMS

Answer TWO questions from this section.

6. (a) State **three** standard signals used to test control signals. (3 marks)
- (b) A servomechanism, when subjected to a unit-step input, has a response described by:
- $$c(t) = 1 + 0.5e^{-30t} - 1.5e^{-10t}$$
- Determine the:
- (i) transfer function;
- (ii) undamped natural frequency;
- (iii) damping ratio. (9 marks)
- (c) A control system has a characteristic equation
- $$S^4 + 6S^3 + 11S^2 + 6S + K = 0$$
- Using Routh's array, determine the range of values of K to ensure the system is stable. (6 marks)
- (d) State **two** limitations of Routh-Hurwitz stability criterion. (2 marks)

7. (a) Define a servo system. (1 mark)
- (b) With the aid of a circuit diagram, describe the use of synchros to detect alignment errors in remote shafts. (8 marks)
- (c) A unity feedback control system has an open-loop transfer function given by:-

$$G_{(s)} = \frac{K}{s(s^2 + 4s + 13)}$$

With respect to root locus technique, determine the following:

- (i) centroid;
- (ii) number of asymptotes;
- (iii) angle asymptotes;
- (iv) angle of departure of roots from poles;
- (v) value of K and frequency at which the root locus crosses the $j\omega$ -axis. (11 marks)
8. (a) Define each of the following with respect to control systems:
- (i) feedback;
- (ii) control element. (2 marks)
- (b) Figure 4 shows a signal flow diagram of a control system.

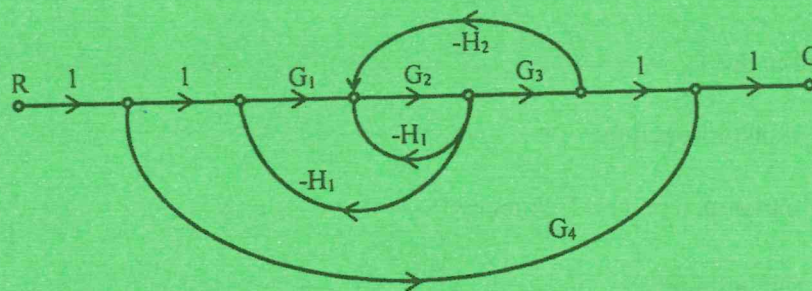


Fig. 4

- (i) Draw a block diagram for the control system.
- (ii) Determine the transfer function using Mason's gain formula. (12 marks)

(c) Figure 5 shows a circuit diagram of an electrical network.

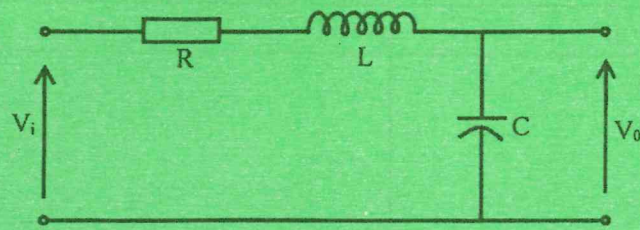


Fig. 5

- (i) Derive the differential equations to describe the network.
- (ii) Determine the expression for the transfer function.

(6 marks)

Table of Laplace transform pairs

$f(t), t > 0$	$f(s)$
$\delta(t)$	1
e^{-at}	$\frac{1}{s+a}$
$\frac{1}{b-a} (e^{-at} - e^{-bt})$	$\frac{1}{(s+a)(s+b)}$
$\text{Sin}\omega t$	$\frac{\omega}{s^2 + \omega^2}$
$\text{Cos}(\omega t)$	$\frac{s}{s^2 + \omega^2}$
t	$\frac{1}{s^2}$
t^2	$\frac{2}{s^3}$
$\frac{1}{\omega} e^{-at} \text{Sin}\omega t$	$\frac{1}{(s+a)^2 + \omega^2}$
1	$\frac{1}{s}$

THIS IS THE LAST PRINTED PAGE.