

2506/202

2507/202

**ELECTRONICS AND CONTROL SYSTEMS**

**June/July 2017**

**Time: 3 hours**



**THE KENYA NATIONAL EXAMINATIONS COUNCIL**

**DIPLOMA IN AERONAUTICAL ENGINEERING  
(AIRFRAMES AND ENGINES OPTION)  
(AVIONICS OPTION)**

**MODULE II**

**ELECTRONICS AND CONTROL SYSTEMS**

**3 hours**

**INSTRUCTIONS TO CANDIDATES**

*You should have the following for this examination:*

*Answer booklet;*

*Non-programmable scientific calculator.*

*This paper consists of **EIGHT** questions in **TWO** sections; **A** and **B**.*

*Answer **THREE** questions from section **A** and **TWO** questions from section **B**.*

*All questions carry equal marks.*

*Maximum marks for each part of a question are as indicated.*

*Candidates should answer the questions in English.*

**This paper consists of 7 printed pages.**

**Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.**



## SECTION A: ELECTRONICS

Answer **THREE** questions from this section.

1. (a) Perform the following conversions:
- (i)  $(1101.11)_2$  into decimal;
  - (ii)  $(47C30.19)_{HEX}$  into binary. (7 marks)
- (b) Figure 1 shows a logic circuit diagram. Derive the Boolean expression for the output.

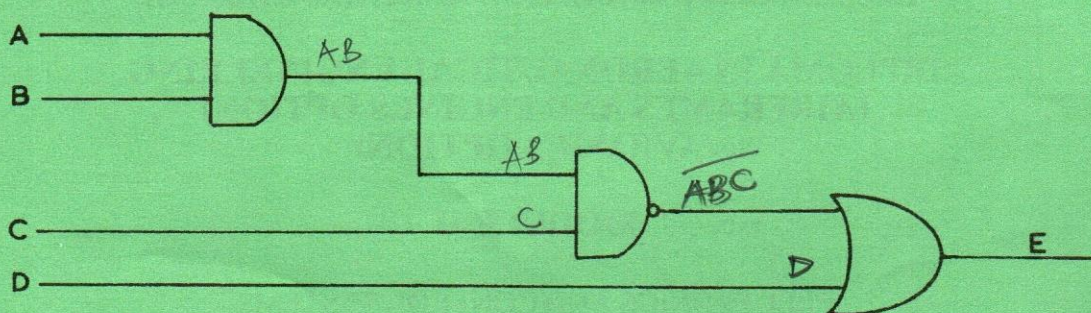


Fig. 1

(3 marks)

- (c) Prove the following Boolean identity:

$$A + \overline{A}B = A + B$$

(4 marks)

- (d) With the aid of a circuit diagram, explain the operation of an RTL logic circuit.

(6 marks)

2. (a) State the essential conditions for maintaining oscillations in an oscillator. (2 marks)
- (b) A quartz crystal resonating at 450 kHz has an equivalent inductance of 4.2 H, an equivalent capacitance of 0.0297 pF, connected in series with a resistance of  $60\ \Omega$ . Determine the:
- (i) equivalent impedance in ohms;
  - (ii) Q factor. (8 marks)
- (c) With the aid of a two transistor analogy of the silicon controlled rectifier, explain the regeneration of current in the device. (6 marks)



(d) A tunnel diode has the following data:

$$I_p = 2 \text{ mA at } V_p = 60 \text{ mV.}$$

$$I_v = 0.15 \text{ mA at } V_v = 350 \text{ mV.}$$

Determine the resistance of the tunnel diode.

(4 marks)

3. (a) With the aid of energy band diagrams, explain conductivity in each of the following:

- (i) conductor;
- (ii) insulator;
- (iii) semiconductor.

(9 marks)

(b) (i) Define an intrinsic semiconductor. *- pure semi-conductors without doping*

(ii) With the aid of a lattice diagram, explain the formation of an N-type semiconductor.

(7 mark)

(c) Figure 2 shows a fixed bias silicon amplifier circuit diagram. Determine the DC voltages at point:

- (i)  $TP_1$ ;
- (ii)  $TP_2$ .

(4 marks)

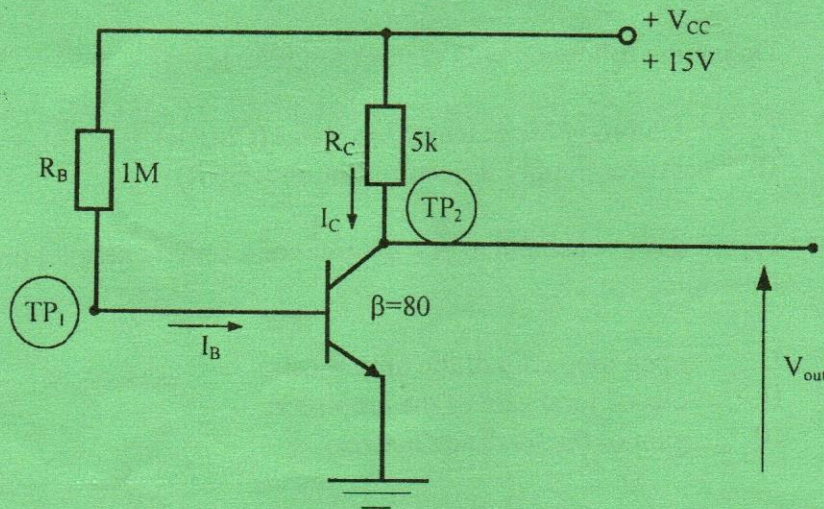


Fig. 2

4. (a) With the aid of a diagram, describe the construction and operation of N-junction Field Effect transistor. (6 marks)

(b) State **three** advantages of FETs over Bipolar transistors. (3 marks)

- 1. High input impedance
- 2. Ruggedness
- 3. Small size



(c) Figure 3 shows a circuit diagram of a voltage stabilizer. The zener diode used in the regulator circuit has a voltage  $V_{in}$  that can be varied from 20 V to 30 V. Determine the:

- (i) minimum and maximum currents in the zener;
- (ii) the minimum and maximum power dissipated in the diode;
- (iii) maximum rated power dissipation that  $R_s$  should have.

Assume the zener diode remains in breakdown.

(11 marks)

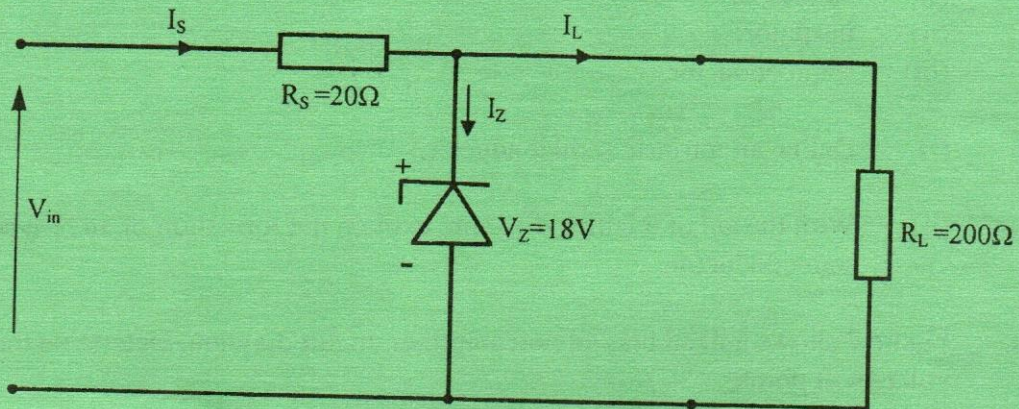


Fig. 3

5. (a) List **four** characteristics of an ideal operational Amplifier (OPAMP). (4 marks)

(b) (i) Define the following with respect to OPAMPs:

- I. Common Mode Rejection Ratio (CMRR);
- II. Power Supply Rejection Ration (PSRR).

(4 marks)

(ii) Figure 4 is a schematic block diagram of a series - parallel feedback amplifier. Determine the:

- I. open loop gain of the amplifier;
- II. closed loop gain of the amplifier;
- III. gain of the feedback network.

(6 marks)



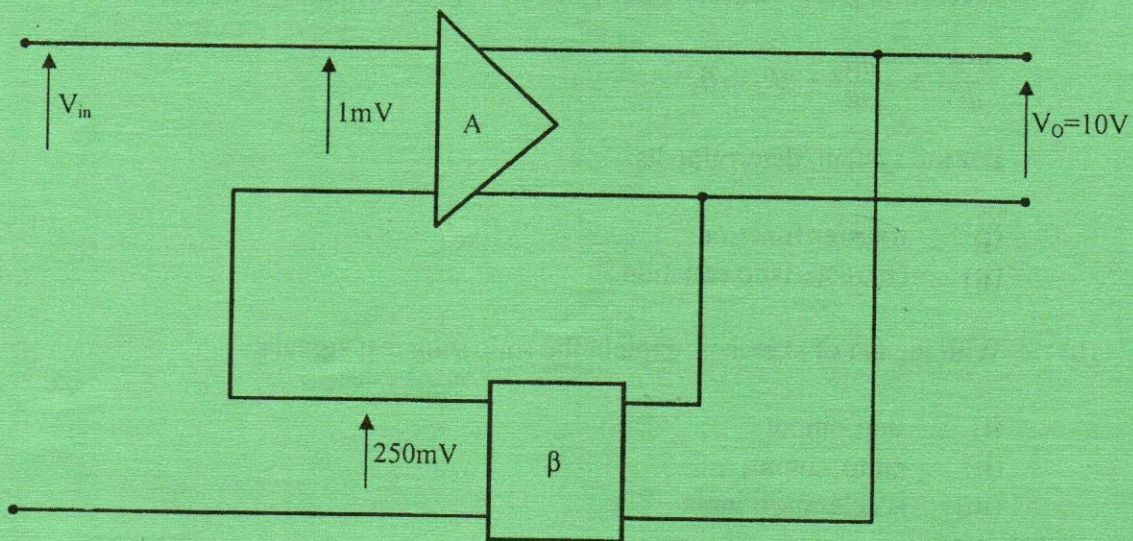


Fig. 4

- (c) With the aid of a circuit diagram, explain the operation of a controlled full wave rectifier. (6 marks)

## SECTION B: ENGINEERING CONTROL SYSTEMS

Answer *TWO* questions from this section.

6. (a) With the aid of block diagrams, explain each of the following control systems:
- open loop;
  - closed loop.
- (8 marks)
- (b) Highlight **four** merits of using closed loop control systems. (4 marks)
- (c) (i) Define 'Transfer Function' as used in control systems.
- (ii) Explain the following as applied in control systems:
- signal flow graphs;
  - forward path;
  - loop gain.
- (8 marks)

23  
-16  
-----  
7  
29  
+2  
-----  
31



7. (a) A control system is described by the differential equation:

$$\frac{d^2\theta_0}{dt^2} + 4\frac{d\theta_0}{dt} + 3\theta_0 = \theta_i$$

For the system, determine its:

- (i) transfer function;
- (ii) characteristic equation.

(6 marks)

- (b) With the aid of sketches, explain the following test signals:

- (i) step - input;
- (ii) ramp - input;
- (iii) acceleration input.

(6 marks)

- (c) (i) Define the following as applied to control systems in system response:

- I. settling time;
- II. overshoot.

- (ii) The characteristic equation of a second order system is given by:

$$S^2 + 0.6S + 9 = 0$$

Determine the:

- I. natural frequency;
- II. damped natural frequency.

(8 marks)



8. (a) Figure 5 shows a circuit diagram of a summing amplifier computing different level voltages. Determine the output,  $e_o$ .

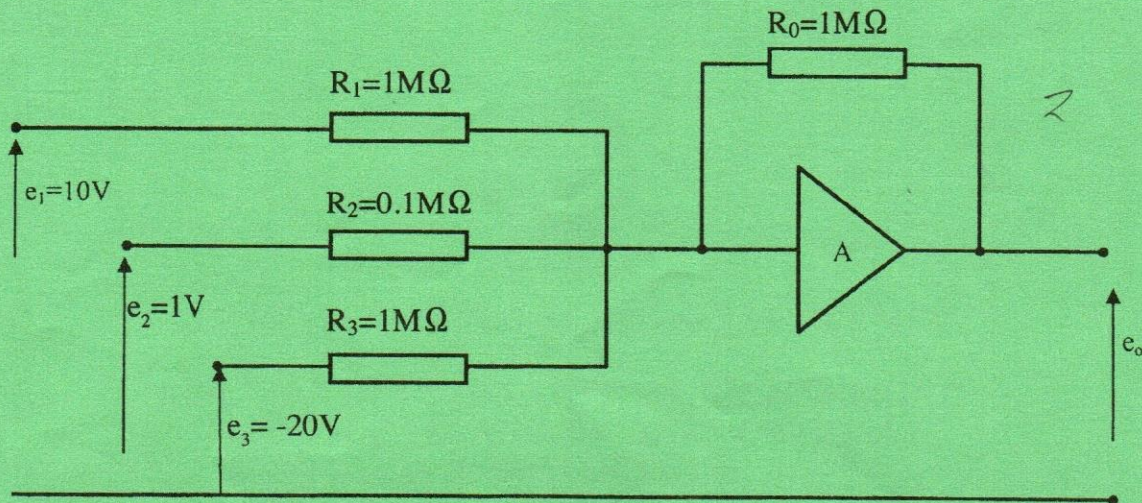


Fig. 5

(4 marks)

- (b) A control system is represented by the equation:

$$\tau \frac{dx}{dt} + x = y;$$

Draw a computer simulation diagram for the system.

(6 marks)

- (c) (i) Define the following with respect to control system stability:

- gain margin ( $G_m$ ) — This is the point on the  $G(f)$  plane where  $G(f)$  has a unity magnitude
- phase margin ( $\phi P_m$ ) — How much the locus is less than  $-180^\circ$  at the gain cross-over

(4 marks)

- (ii) With the aid of a diagram, describe the construction of a synchro transmitter - receiver system.

(6 marks)

**THIS IS THE LAST PRINTED PAGE.**