

2207/302

TELECOMMUNICATION PRINCIPLES

Oct./Nov. 2010

Time: 3 hours

THE KENYA NATIONAL EXAMINATIONS COUNCIL
DIPLOMA IN AERONAUTICAL ENGINEERING AVIONICS
(COMMUNICATION AND NAVIGATION OPTION)

TELECOMMUNICATION PRINCIPLES

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Smith chart;

Mathematical tables/Scientific calculator.

*Answer any **FIVE** of the **EIGHT** questions in this paper.*

All questions carry equal marks.

Maximum marks for each part of a question are as shown.

This paper consists of 8 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

© 2010 The Kenya National Examinations Council

Turn over

1. (a) For the diode clipper circuit shown in figure 1:

- (i) describe its operation;
- (ii) sketch the output voltage waveform for a sinusoidal input voltage.

Assume negligible diode forward drop.

(6 marks)

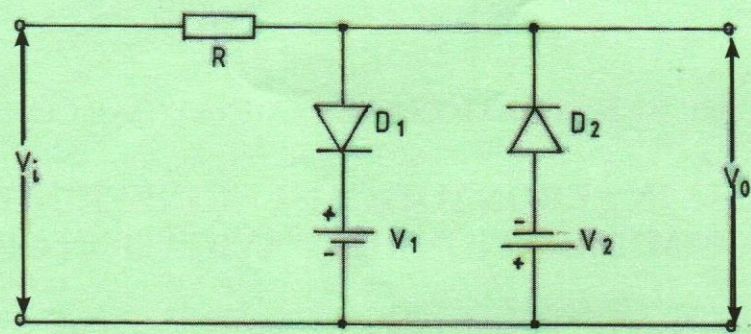


FIG. 1

(b) Obtain the expression for the cutoff frequency of the filter circuit shown in figure 2.

(4 marks)

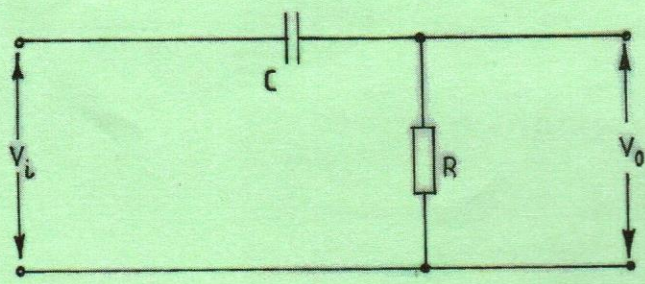


FIG. 2

(c) (i) Draw the circuit diagram of a transistor R-C phase-shift oscillator and describe its operation.

(ii) The oscillator in c(i) has a collector resistor, $R_c = 10k\Omega$, resistance seen looking into the base, $R = 8k\Omega$ and phase shift capacitors $C_1 = C_2 = C_3 = C$. Determine the value of the:

- I. capacitor C to provide oscillating frequency of 2kHz;
- II. transistor current gain, h_{fe} , to provide sufficient loop gain for oscillations to start.

(10 marks)

2. (a) (i) State any **three** areas of application of varactor diodes. (8 marks)
- (ii) Sketch the characteristic curve of the diode in a(i) and explain its shape. (6 marks)
- (b) With the aid of a labelled diagram describe the operation of a capacitive transducer employed in liquid level measurement. (6 marks)
- (c) A copper-constantan thermocouple, with reference junction temperature of 0°C , has a linear calibration between 0°C to 400°C with e.m.f. at maximum temperature equal to 20.68mV . If the reference junction temperature changes to 25°C , determine the:
- (i) sensitivity of the thermocouple in $\text{mV}/^{\circ}\text{C}$;
- (ii) temperature of the hot junction if the indicated e.m.f is 8.92mV . (6 marks)

3. (a) (i) State any **two** advantages of diode - over transistor - detectors in amplitude modulated (AM) systems. (7 marks)
- (ii) Describe the operation of the circuit shown in figure 3. (7 marks)

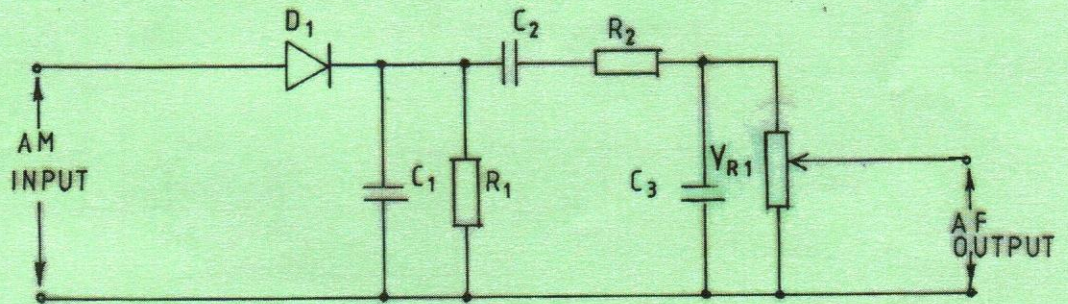


FIG. 3

- (b) For an AM wave, obtain the expression for the total power in terms of the carrier power and the modulation index. (7 marks)

- (c) An AM transmitter radiates 8.91 kW with the carrier unmodulated and 10.25 kW when the carrier is sinusoidally modulated. If the carrier is modulated to a depth of 40% by another sine wave, determine the:
- total modulation index;
 - total power radiated;
 - percent saving in power when the carrier and one sideband are suppressed.

(6 marks)

4. (a) (i) State any **two** advantages of frequency modulation (FM) over amplitude modulation (AM) systems.
- (ii) With the aid of a labelled block diagram describe the operation of a direct-modulation FM transmitter employing automatic frequency control (AFC).
- (b) Describe the operation of the Foster-Seeley detector circuit shown in figure 4, hence sketch its response curve.

(9 marks)

(5 marks)

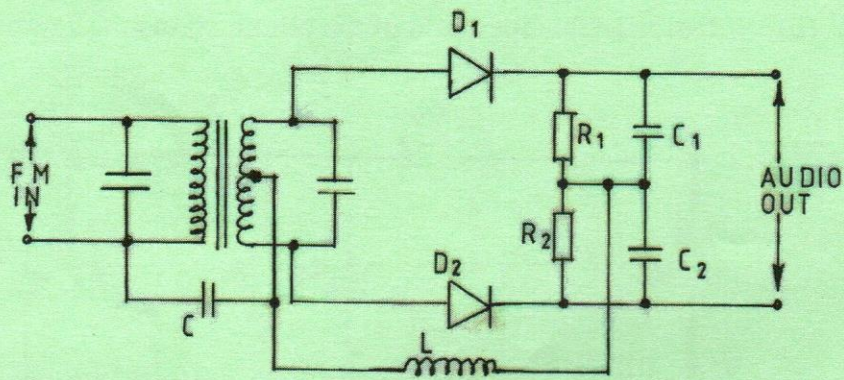


FIG. 4

- (c) A carrier wave, when frequency modulated by a 2.4V, 500Hz sinusoidal signal, gives a deviation of 4.8 kHz. If the modulating signal voltage is increased to 7.2V, determine the:
- new deviation;
 - change in modulation index.

(6 marks)

5. (a) For the small signal amplifier shown in figure 5,

- (i) draw the h-parameter equivalent circuit ignoring h_{re} and h_{oe} ;
- (ii) determine the voltage gain for the circuit in a(i) given that $h_{fe} = 50$ and $h_{ie} = 1k\Omega$

(8 marks)

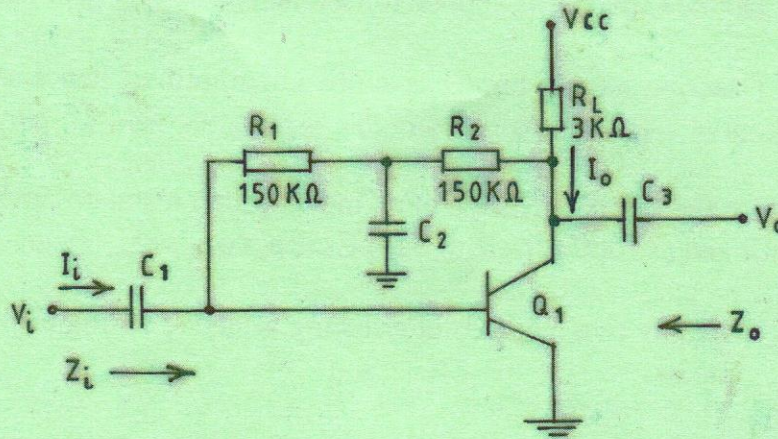


FIG 5

- (b) (i) State any **two** advantages of push-pull over single-ended operation of power amplifiers.
- (ii) Figure 6 is a circuit diagram of a complementary-symmetry class B power amplifier. Given that the input signal voltage, $V_i = 12 V_{rms}$ and the voltage gain, $A_v = 1$, determine the:

- I. a.c. output power;
- II. d.c. input power;
- III. amplifier efficiency.

(12 marks)

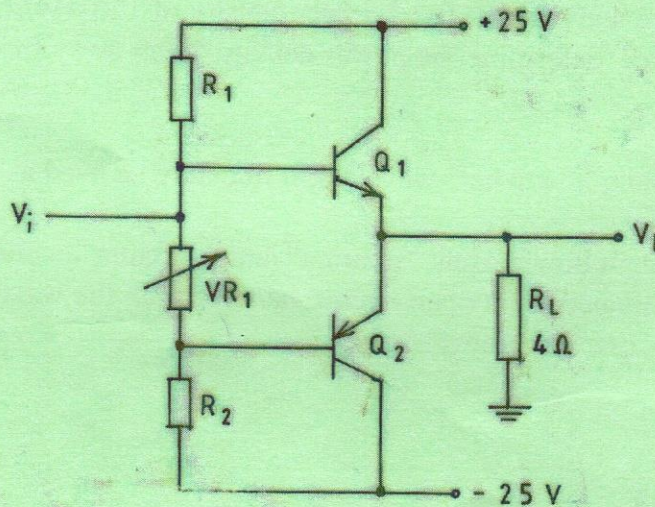


FIG. 6

6. (a) (i) State any **two** effects of applying negative feedback to amplifiers.
- (ii) An amplifier has a voltage gain of 1000 without feedback. If 3% of the output voltage is applied as negative feedback, determine the change in gain with feedback when the gain without feedback falls by 50%. (6 marks)
- (b) (i) Define Q-factor as applied to resonant circuits.
- (ii) Describe stagger-tuning as applied to amplifiers hence sketch the response curve. (7 marks)
- (c) Determine the self capacitance of an inductor that resonates at 500kHz with a 100pF capacitor and at 1000 kHz with a 20pF capacitor. (7 marks)
7. (a) (i) State any **two** methods of reducing selective fading in sky wave communication systems.
- (ii) With the aid of a labelled diagram describe the fading in a(i). (7 marks)
- (b) With the aid of a labelled diagram explain atmospheric ducting with respect to radio wave propagation. (5 marks)
- (c) (i) An electromagnetic wave travelling in free space is refracted when it enters the ionosphere such that the original angle of 35° changes to 25° . Determine the:
- I. refractive index of the ionosphere;
- II. velocity of the wave in the ionosphere.
- (ii) If the wave in c(i) has a power density of $150 \mu\text{W}/\text{m}^2$ at 30km from a point source, determine the power density 40km away from the source. (8 marks)
8. (a) (i) Explain how a half-wavelength line may be used as a band-stop filter.
- (ii) Explain how current “minima” and “maxima” occur in a transmission line terminated in an open circuit, hence sketch the wave pattern. Assume a loss free line, one wavelength long. (8 marks)

- (b) A 50Ω transmission line has a voltage standing wave ratio of 2 when an unknown load is connected to its output terminals and produces voltage minima 30cm apart. When the unknown load is removed and replaced by a short-circuit, the voltage minima moves by 7.5cm. Using the Smith chart, determine the impedance of the unknown load. (4 marks)
- (c) If the load in (b) is now connected to a 75Ω transmission line, determine the following using the Smith chart:
- point, nearest the load, at which $\frac{\lambda}{4}$ transformer may be inserted to provide correct matching;
 - characteristic impedance of the transformer. (8 marks)

IMPEDANCE OR ADMITTANCE COORDINATES

