

2207/302

TELECOMMUNICATION PRINCIPLES

Oct./Nov. 2011

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**DIPLOMA IN AERONAUTICAL ENGINEERING AVIONICS
(COMMUNICATION AND NAVIGATION OPTION)**

TELECOMMUNICATION PRINCIPLES

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Mathematical table/scientific calculator.

*Answer any **FIVE** of the **EIGHT** questions in this paper.*

All questions carry equal marks.

Maximum marks for each part of a question are as shown.

This paper consists of 5 printed pages.

**Candidates should check the question paper to ascertain that
all the pages are printed as indicated and that no questions are missing.**

1. (a) (i) State how the following line parameters arise in a transmission line:
- I. inductance, L ;
 - II. capacitance, C ;
 - III. conductance, G .
- (ii) Describe how a $\frac{\lambda}{4}$ transformer may be used to match a load to a transmission line. (7 marks)
- (b) A lossless transmission line having a characteristic impedance $Z_0 = 75\Omega$ is terminated in a resistive load of impedance $Z_L = 250\Omega$. If the voltage across the terminating load is 15V, determine the:
- (i) reflection coefficient for the line;
 - (ii) incident current;
 - (iii) reflected voltage. (13 marks)
2. (a) (i) State the frequency band for each of the following radio waves:
- I. low frequency (l.f.)
 - II. super high frequency (s.h.f)
- (ii) With the aid of a labelled diagram describe space wave communication. (7 marks)
- (b) Explain the importance of maximum usable frequency (m.u.f) in the propagation of radio waves. (5 marks)
- (c) An electromagnetic wave is refracted when it enters an ionospheric layer having a maximum electron density of 2×10^{10} electrons/m³. If the angle of incidence is 60° and the refractive index is 1.5, determine the:
- (i) angle of refraction;
 - (ii) maximum frequency that can be returned to earth;
 - (iii) critical frequency. (8 marks)
3. (a) (i) State any **two** advantages of single sideband (SSB) over double sideband (DSB) systems.
- (ii) With the aid of a labelled block diagram describe the phase shift method of generating an SSB signal. (8 marks)
- (b) With the aid of waveforms explain how a pulse position modulated (PPM) signal is obtained from a pulse width modulated (PWM) signal. (7 marks)

(c) A carrier wave is amplitude modulated (AM) to a depth of 50%. If the carrier and one sideband are suppressed in the AM wave, determine the percentage saving in the transmitted power. (5 marks)

4. (a) (i) State the **two** conditions that are necessary for oscillation to be sustained in an oscillator.
 (ii) With the aid of a circuit diagram describe the operation of a tuned-collector sinusoidal oscillator. (8 marks)

(b) Figure 1 shows the circuit diagram of the frequency determining network of a colpitts oscillator. Derive the expression for the oscillation frequency. (6 marks)

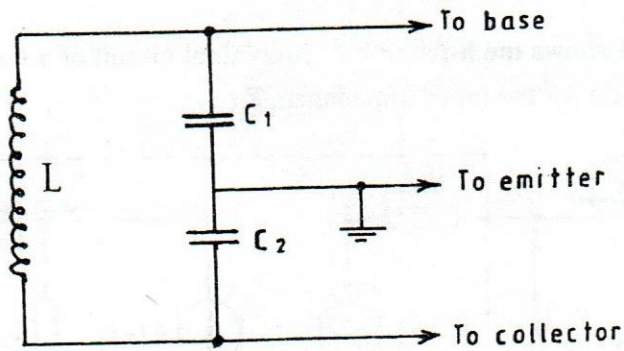


Fig. 1

(c) Figure 2 shows the circuit diagram of a Schmitt trigger. Determine the value of the hysteresis voltage. (6 marks)

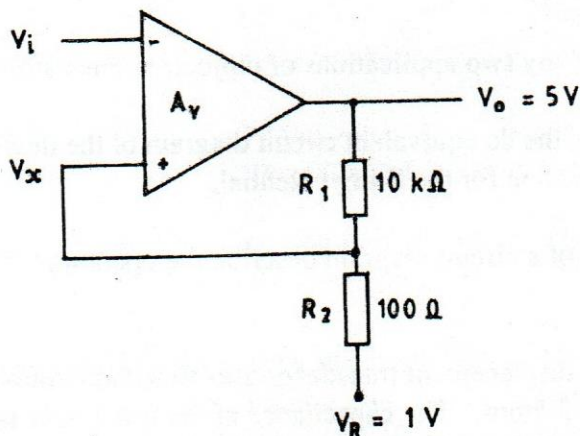


Fig. 2

5. (a) (i) Distinguish between class A and class B biasing of power amplifiers.
- (ii) A class B push-pull power amplifier takes a mean current of 2.2A from a 30V supply. The output transformer has a turns ratio of 5:1 and feeds a load of 10Ω . The current gain of each transistor is 50. If a sinusoidal signal of 8.5mA(rms) is applied to the base of each transistor determine the:
- I. optimum load resistance for each transistor;
 - II. total power output;
 - III. efficiency of the amplifier.

(14 marks)

- (b) Figure 3 shows the h-parameter equivalent circuit of a transistor. Derive the expression for the input impedance, Z_i .

(6 marks)

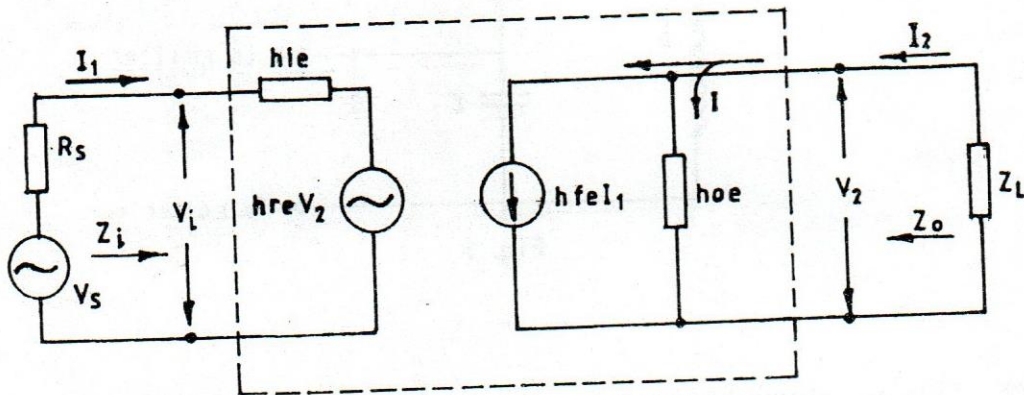


Fig. 3

6. (a) (i) State any two applications of unijunction transistor (UJT).
- (ii) Draw the dc equivalent circuit diagram of the device in a(i) hence obtain the expression for the firing potential. (7 marks)
- (b) With the aid of a circuit diagram describe the operation of the repulsion type induction motor. (6 marks)
- (c) A capacitive displacement transducer uses two diaphragms of area 750mm^2 separated by a distance of 3.5mm. The capacitance of the transducer is 370pF with no pressure applied to the diaphragms. If a pressure of 900KN/m^2 is applied to the top diaphragm determine the:
- (i) new capacitance;
 - (ii) sensitivity of the transducer.

(7 marks)

7. (a) (i) State any **two** disadvantages of frequency modulation (FM) as compared to amplitude modulation (AM) systems.
- (ii) With the aid of a circuit diagram describe the operation of a varactor diode FM modulator. (7 marks)
- (b) Explain how changes in the amplitude of the modulating signal affect the bandwidth of an FM signal. (4 marks)
- (c) An FM wave is represented by the expression:
 $v = 4 \sin (1.57 \times 10^8 t + 25 \sin 2513t)$ volts. Determine the:
- (i) carrier frequency;
(ii) modulating signal frequency;
(iii) maximum deviation;
(iv) bandwidth. (9 marks)
8. (a) (i) State any **two** effects of a high value of Q in a parallel resonant circuit.
- (ii) Explain the need for a damping resistor in a tuned circuit. (6 marks)
- (b) The winding of a double-tuned transformer are identical, each having a self inductance of $720\mu\text{H}$ and tuned to resonance by a loss free capacitor of 100pF . If the 3B bandwidth of the transformer is 10kHz and the mutual inductance between the two windings is $8.5\mu\text{H}$, determine the:
- (i) resonant frequency;
(ii) Q - factor;
(iii) coefficient of coupling. (7 marks)
- (c) An amplifier has a gain of 1000 and 0.1 of the output voltage is applied as negative feed back. Determine the change in:
- (i) bandwidth;
(ii) distortion;
(iii) gain due to a temperature change of 20%. (7 marks)