

2507/207

ELECTRIC CIRCUIT ANALYSIS

June/July 2023

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**DIPLOMA IN AERONAUTICAL ENGINEERING
(AVIONICS OPTION)**

MODULE III

ELECTRIC CIRCUIT ANALYSIS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Non-programmable scientific calculator;

Drawing instruments.

*This paper consists of **EIGHT** questions.*

*Answer **FIVE** questions in the answer booklet provided.*

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 5 printed pages.

**Candidates should check the question paper to ascertain that
all the pages are printed as indicated and that no questions are missing.**

1. (a) Define each of the following quantities with respect to symmetrical two-port networks:


- (i) Characteristic impedance;
- (ii) Propagation coefficient (γ);
- (iii) Insertion loss.

(3 marks)

(b) **Figure 1** shows a T two-port network. Determine the expressions of each of the following:

- (i) $\tanh \gamma$;
- (ii) Z_{oc} ;
- (iii) Z_{sc} .


(6 marks)

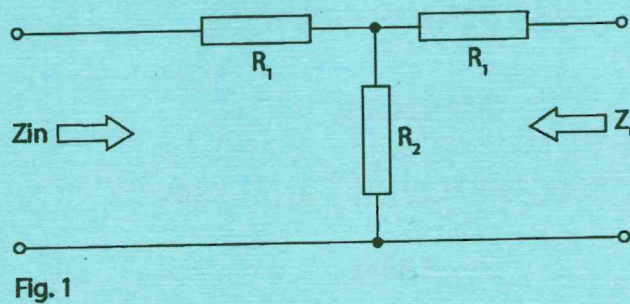

(c) **Figure 2** shows a π two-port network. Determine the:

- (i) characteristic impedance, Z_o ;
- (ii) insertion loss if the input power is 2 kW and output voltage and current is 8 V and 2 A respectively.

(9 marks)

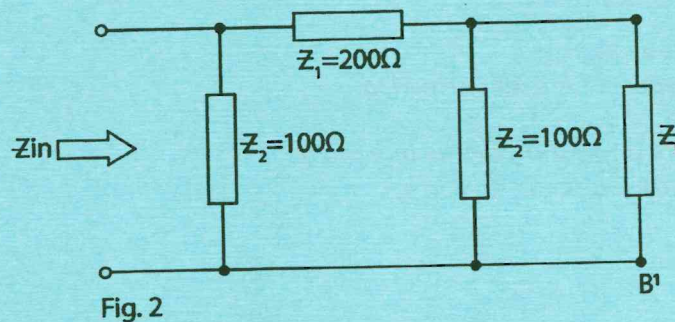

(d) Explain an asymmetrical network as applied to two-port networks.


(2 marks)

2. (a) With the aid of a labelled diagram, explain the construction of a d.c machine. (8 marks)
- (b) A 6-pole d.c lap-wound shunt motor is connected to a 240 V d.c source. The resistance of the armature is 2Ω and has 400 conductors. The magnetic flux produced is 20 mWb per pole. If the armature current is 50 A, determine the:
- back e.m.f;
 - speed;
 - torque.
- (8 marks)
- (c) Sketch each of the following characteristic curves for a d.c series motor:
- speed-armature current;
 - torque-armature current.
- (4 marks)
3. (a) State **three** merits of a capacitor start capacitor run motor. (3 marks)
- (b) With the aid of a labelled diagram, explain the operation of a shaded-pole single phase motor. (6 marks)
- (c) Describe how a single phase induction motor can be modified to be self starting motor. (4 marks)
- (d) A 240 V, 50 Hz, 250 W capacitor-start single phase motor has the following impedances:
- main winding $Z_m = (4 + j3) \Omega$;
 - Auxiliary winding $Z_a = (9 + j3) \Omega$
- Determine the value of the starting capacitor that will place the main winding and auxiliary winding currents in quadrature at starting. (7 marks)

4. (a) List **three** merits of using three phase transformers. (3 marks)
- (b) A 3-phase, 22 kV/300 V, 50 Hz delta-star connected transformer is connected to a balanced star connected three phase load at 0.8 power factor lagging. The line current on the primary is 6 A.
- (i) Draw the connection diagram;
- (ii) Determine the:
- (I) current in each coil of primary and secondary.
- (II) output of the transformer. (10 marks)
- (c) With the aid of a labelled circuit diagram, describe the open-circuit test of a single phase transformer. (7 marks)
5. (a) Describe the production of torque in a three phase induction motor. (5 marks)
- (b) A 3 phase, 50 Hz, induction motor has 4 slots per pole per phase. Determine the:
- (i) number of stator poles produced;
- (ii) total number of slots on the stator;
- (ii) speed of the rotating magnetic field. (6 marks)
- (c) With the aid of a labelled diagram describe the operation of a star-delta starter for the three phase induction motor. (7 marks)
- (d) State **two** applications of three phase synchronous machine. (2 marks)
6. (a) List **three** characteristics of three phase synchronous machines. (3 marks)
- (b) With the aid of a labelled connection diagram, describe the pony motor starting of synchronous machines. (6 marks)
- (c) A 10 pole, 600 V, 50 Hz, 3 phase star connected synchronous motor is operating at no load with normal excitation. It has armature resistance of 10Ω per phase. The rotor is retarded by 0.5° (mechanical) from its synchronous position. Determine the:
- (i) rotor displacement in electrical degrees;
- (ii) phase voltage;
- (iii) armature e.m.f per phase. (8 marks)
- (d) With the aid of a diagram, show how a three phase synchronous machine is synchronised using the lamps dark method. (3 marks)

7. (a) With the aid of a labelled diagram, describe the two-wattmeter method of power measurement. (6 marks)
- (b) With the aid of a labelled diagram, describe the 3-phase 4-wire system. (6 marks)
- (c) A balanced 3 phase, 3 wire system with star connected load has a line voltage of 240 V. The impedance of each phase is $(4 + j 5)$ ohms. Determine the:
- magnitude of phase impedance;
 - phase voltage;
 - phase current;
 - power absorbed by the phase load.
- (8 marks)
8. (a) State Thevenin's theorem. (2 marks)

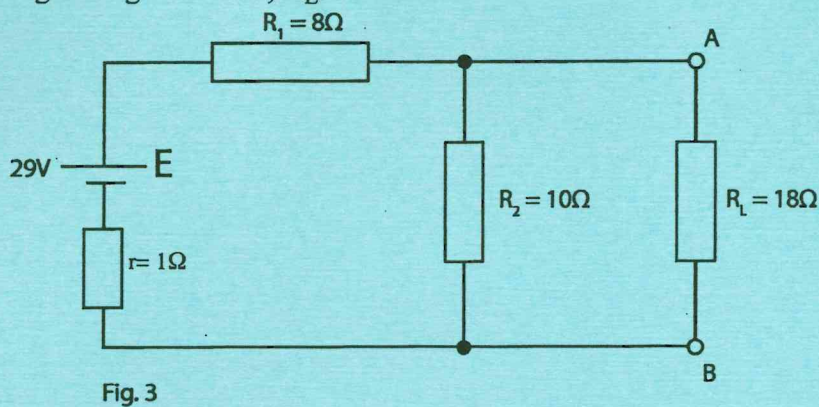- (b) **Figure 3** shows a resistive network. Using Thevenin's theorem, determine the current flowing through the load, R_L . (8 marks)



- (c) An e.m.f represented by the equation $e = 150 \sin 314t + 60 \sin 942t$ volts is applied to a capacitor having a capacitance of $31 \mu F$. Determine the:
- capacitive reactive due to fundamental frequency;
 - amplitude of the fundamental current;
 - amplitude of the 3rd harmonic current.
- (7 marks)
- (d) Define each of the following transients:
- Initiation transients;
 - Subsidence transients;
 - Transition transients.
- (3 marks)

THIS IS THE LAST PRINTED PAGE.