

2506/202
2507/202
ELECTRONICS AND CONTROL SYSTEMS
June/July 2023
Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL
DIPLOMA IN AERONAUTICAL ENGINEERING
(AIRFRAMES AND ENGINES OPTION)
(AVIONICS OPTION)

MODULE II

ELECTRONICS AND CONTROL SYSTEMS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Mathematical tables / Non-programmable scientific calculator;

Log-linear graph paper;

Drawing instruments.

This paper consists EIGHT questions in TWO sections; A and B.

Answer THREE questions from section A and TWO questions from section B in the answer booklet provided.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 8 printed pages and 1 insert.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

SECTION A: ELECTRONICS

Answer **THREE** questions from this section.

1. (a) Perform each of the following number system conversions:

(i) $(827)_{10}$ into:

(I) 8421 BCD;

(II) 5211 BCD.

(ii) $(629)_{10}$ into:

(I) Octal;

(II) Binary;

(III) Hexadecimal.

(10 marks)

(b) Perform each of the following operations:

(i) $(110011)_2$
 $\times (101101)_2$

(ii) $(17)_{10} - (169)_{10}$ in two's complement using 9-bits. Leave the result in binary. (6 marks)

(c) A half-subtractor consists of two inputs, A and B and two outputs D and Bo. Draw the truth table for the circuit. (4 marks)

2. (a) Define each of the following with respect to atomic structure of elements:

(i) covalent bond;

(ii) energy band.

(2 marks)

(b) With aid of an energy-level diagram, explain a p-type semiconductor. (5 marks)

(c) A sample of silicon is made N-type by addition of pentavalent atoms at a rate of 1 atom per 8×10^6 silicon atoms. The intrinsic carrier concentration in silicon is, $n_i = 4 \times 10^{16} / m^3$ and the number of silicon atoms per unit volume is $22 \times 10^{28} / m^3$. Determine the:

(i) concentration of donor atoms;

(ii) concentration of electrons in the conduction band;

(ii) concentration of holes in the valency band.

(6 marks)

- (d) (i) Draw the V-I characteristic curve of a unijunction transistor (UJT) and label the **three** distinct regions.
- (ii) State **two** applications of UJT. (7 marks)
3. (a) Define each of the following with respect to flip-flops:
- (i) set-up time;
- (ii) hold time. (2 marks)
- (b) (i) Draw the truth table for SR-flip flop.
- (ii) Draw the logic circuit diagram of a JK-flip flop, made from SR-flip flop and gates. (6 marks)
- (c) For a modulo-12 Asynchronous up counter:
- (i) Draw the counting sequence;
- (ii) Determine the number of JK flip flops required;
- (iii) Draw the schematic block diagram of the counter. (9 marks)
- (d) A $4K \times 8$ memory is made from $2K \times 4$ memory chips. Determine the:
- (i) number of $2K \times 4$ chips required.
- (ii) size of decoder required for the memory implementation. (3 marks)
4. (a) Define each of the following with respect to PN-diode:
- (i) Depletion region;
- (ii) peak-inverse voltage (PIV). (2 marks)

- (b) Figure 1 shows a circuit diagram of a half-wave diode rectifier supplied from 220 V, 50 Hz through a step-down transformer of turns ratio 20:1. The load resistor, $R_L = 500 \Omega$.

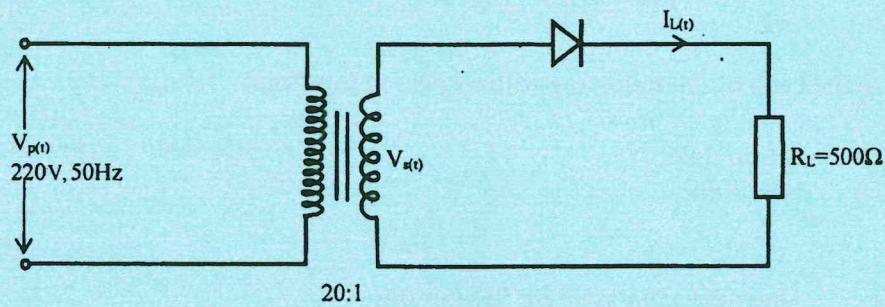


Fig. 1

Assuming the diode is ideal, determine the:

- (i) dc voltage across the load;
- (ii) average output load power;
- (iii) PIV of the diode;
- (iv) ripple factor.

(8 marks)

- (c) State **two** limitations of half-wave rectifiers.

(2 marks)

- (d) (i) Draw the V-I characteristics of a TRIAC and explain its operation.
(ii) State **two** areas of application of TRIAC.

(8 marks)

5. (a) Define each of the following with respect to OP-Amps:

- (i) slew rate;
- (ii) input offset voltage;
- (iii) common-mode rejection ratio.

(3 marks)

- (b) Figure 2 shows a diagram of an OP-Amp based circuit.

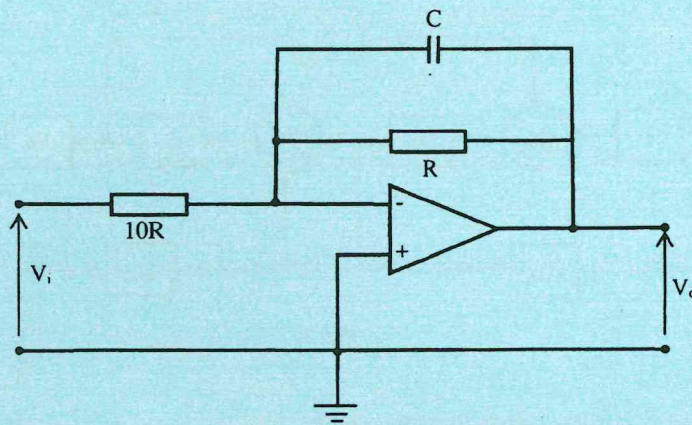


Fig. 2

- (i) Derive the expression for the gain, $\frac{V_o}{V_i}$.
- (ii) Sketch the variation of gain with frequency. (7 marks)
- (c) Draw a circuit diagram of a Colpitts oscillator and explain its operation. (6 marks)
- (d) A Hartley Oscillator tank circuit has a capacitance of 150 pF. The inductances are $L_1 = 2000 \mu\text{H}$ and $L_2 = 200 \mu\text{H}$. Determine the:
- (i) effective oscillator inductance;
- (ii) frequency of oscillation. (4 marks)

SECTION B: CONTROL SYSTEMS

Answer *TWO* questions from this section.

6. (a) Define each of the following with respect to control systems:
- (i) stimulus;
- (ii) plant;
- (iii) disturbance. (3 marks)

(b) Figure 3 shows a block diagram of a control system.

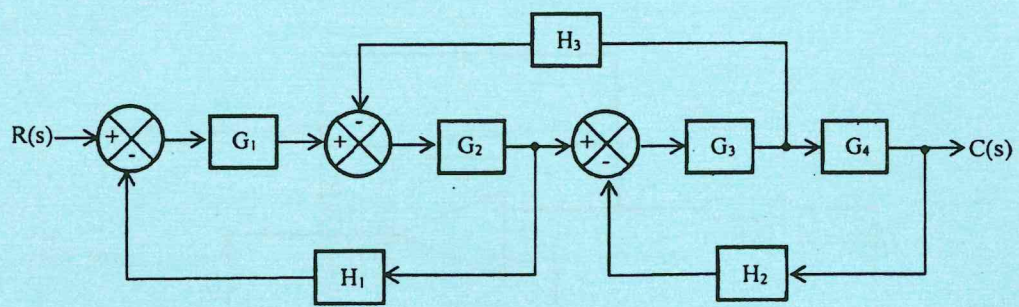


Fig. 3

(i) Draw the signal flow graph for the system.

(ii) Using Mason's gain formula, determine the transfer function, $\frac{C(s)}{R(s)}$. (11 marks)

(c) Figure 4 shows a mass-spring system.

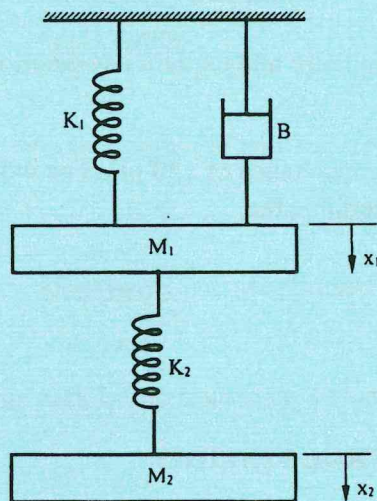


Fig. 4

(i) Write the differential equation to describe the system.

(ii) Draw a circuit diagram for the force-voltage analogy for the system.

(6 marks)

7. (a) (i) Describe the Routh-Hurwitz stability criterion.
(ii) The characteristic equation of a control system is given by:

$$D(s) = 2s^3 + 6s^2 + 6s + K + 1 = 0.$$

Determine the range of K for which the system is stable.

(12 marks)

- (b) A closed-loop servo system is represented by the differential equation:

$$\frac{d^2\theta}{dt^2} + 8\frac{d\theta}{dt} = 64e$$

where e is the displacement of the output shaft and r is the displacement of the input shaft. Where $e = r - \theta$. Determine the:

- (i) undamped natural frequency;
(ii) percentage maximum overshoot for a step input.

(8 marks)

8. (a) Define each of the following with respect to control system stability:

- (i) gain margin;
(ii) phase margin.

(2 marks)

- (b) An open-loop transfer function of a unity feedback control system is given by:

$$G(s) = \frac{80}{(2+s)(4+s)(10+s)}$$

- (i) Determine the corner frequencies.
(ii) Table 1 shows the phase angles at selected frequencies.

Freq (ω) rad/s	0.1	0.5	1.0	2.0	4.0	5.0	8.0	9.0	20	50
Phase angle ($^\circ$)	-4.87	-24.03	-	-82.9	-130	-146	-175	-	-226	-252

Determine the phase angles at frequencies $\omega = 1.0$ and 9 rad/s respectively.

- (iii) Plot the Bode diagram, using asymptotic approximations for gain.

(iv) From the Bode diagram, determine the phase margin of the system. (12 marks)

(c) A control system is represented by the following simultaneous equations:

$$\dot{y} + 4y + x = 3$$

$$\dot{x} + 3x - y = 7$$

Draw an analogue computer flow diagram for simulating the control system. (6 marks)

THIS IS THE LAST PRINTED PAGE.