

2506/202
2507/202
ELECTRONICS AND CONTROL SYSTEMS
Oct/Nov 2023
Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL
DIPLOMA IN AERONAUTICAL ENGINEERING
(AIRFRAMES AND ENGINES OPTION)
(AVIONICS OPTION)

MODULE II

ELECTRONICS AND CONTROL SYSTEMS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Mathematical tables / Non-programmable scientific calculator;

Drawing instruments.

This paper consists EIGHT questions in TWO sections; A and B.

Answer THREE questions from section A and TWO questions from section B in the answer booklet provided.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 9 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

SECTION A: ELECTRONICS

Answer **THREE** questions from this section.

1. (a) Distinguish between:
- (i) intrinsic and extrinsic semiconductors;
 - (ii) majority and minority charge carriers. (4 marks)

- (b) The voltage-ampere equation of a semiconductor diode is given by

$$i_D = I_0 \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

- (i) Identify each parameter.
- (ii) Sketch the diode characteristic.
- (iii) Derive the expression for the dynamic resistance of the diode,

$$\frac{dV_D}{di_D} \quad (8 \text{ marks})$$

- (c) (i) With aid of a sketch, describe transistor load line and state its significance.
(ii) Differentiate biasing of class A and class B push-pull transistor amplifiers. (8 marks)

2. (a) Perform each of the following arithmetic operations in the given number systems:

(i) $(AFCD)_{16} + (9AAC)_{16}$;

(ii) $(467)_8 - (276)_8$;

(iii) $0111\ 1001_{BCD} + 0011\ 0111_{BCD}$ (6 marks)

- (b) Simplify each of the following Boolean expressions:

(i) $(D + \overline{E})(D + E)$

(ii) $WXY + W\overline{X}Y + WX\overline{Y} + W\overline{X}\overline{Y}$. (6 marks)

- (c) Table 1 shows the truth table of a 2-bit multiplier with inputs A_1A_0, B_1B_0 and output $P_3P_2 P_1P_0$.

- (i) Complete the truth table.
- (ii) Draw a logic circuit diagram to implement the multiplier using 3-to-8 decoders and gates. (8 marks)

Table 1

Input				Output			
A_1	A_0	B_1	B_0	P_3	P_2	P_1	P_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	-	-	-	-
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	-	-	-	-
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	-	-	-	-
1	0	1	0	0	1	0	0
1	0	1	1	0	0	1	1
1	1	0	0	0	0	0	0
1	1	0	1	-	-	-	-
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

3. (a) Define a transistor model. (1 mark)

(b) Figure 1 shows a circuit diagram of a common-emitter amplifier. The silicon transistor Q has $\beta = 200$, $V_{BE} = 0.7V$ and the resistance of the emitter diode $r = \frac{25}{I_E(mA)} \Omega$.

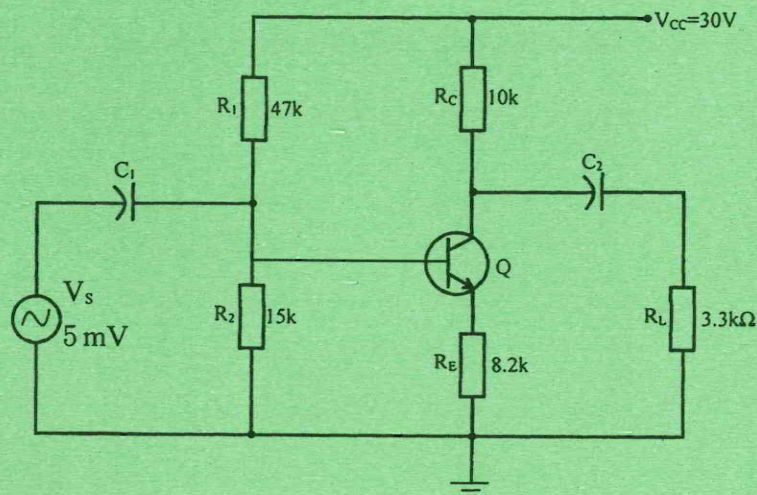


Fig. 1

- (i) Draw the equivalent circuit diagram of the amplifier.
- (ii) Determine the:
- I. Thevenin input voltage;
 - II. Thevenin input resistance;
 - III. emitter-base diode resistance, r_e
 - IV. output a.c load resistance;
 - V. voltage gain. (13 marks)
- (c) Briefly describe the working of each of the following display devices:
- (i) cathode ray tube (CRT);
 - (ii) liquid crystal display (LCD). (6 marks)
4. (a) Define each of the following with respect to analog-to-digital converters (ADCs):
- (i) conversion speed;
 - (ii) monotonicity. (2 marks)
- (b) With aid of a block -schematic diagram, describe the counter-based ADC. (6 marks)
- (c) A 32 KX8 RAM is made from 8KX8 RAM chips. The RAM memory starts form address 1000H.
- (i) Determine the:
- I. number of RAM chips required;
 - II. memory address range of each RAM chip;
 - III. size of decoder required.
- (ii) Draw a schematic block diagram of the memory implementation. (12 marks)
5. (a) State **three** advantages of field effect transistors (FETs) over bipolar junction transistors (BJTs). (3 marks)

(b) Figure 2 shows the characteristic curve of a MOSFET.

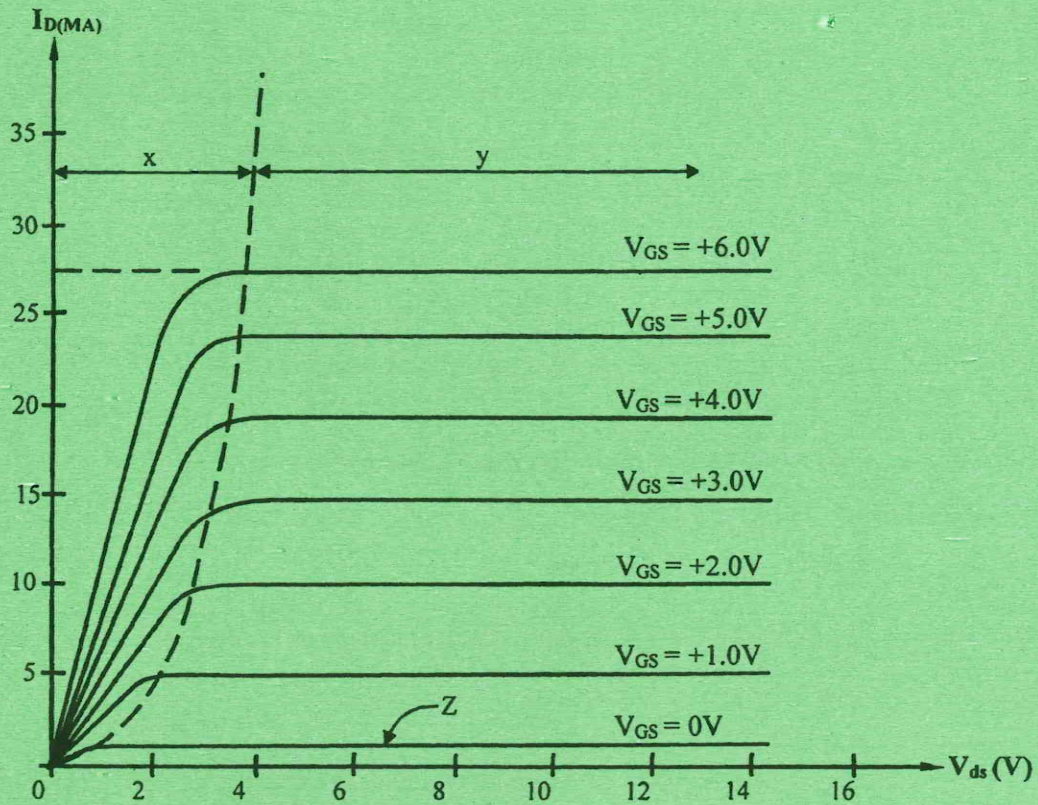


Fig. 2

- (i) Identify the regions labelled x, y and z and explain their significance.
- (ii) Distinguish between enhanced and depletion modes of operating MOSFETs.

(8 marks)

- (c) Figure 3 shows a block diagram of a negative feedback amplifier where A is the gain without feedback and β is the feedback factor.

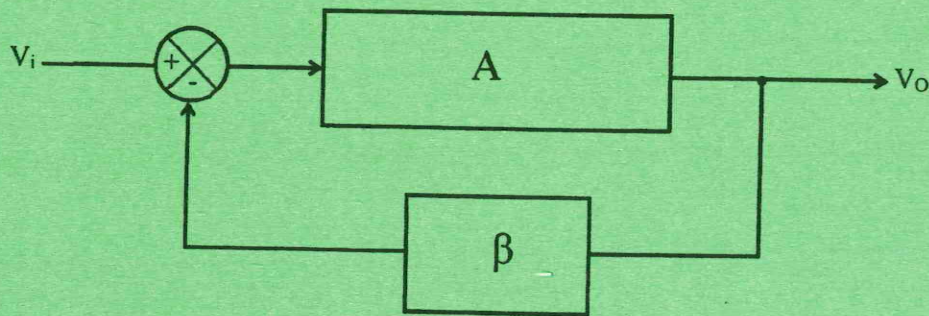


Fig. 3

- (i) Derive the expression of the gain with feedback.
- (ii) An amplifier has a gain of 1000 and a negative feedback of 0.22. Determine the voltage gain with feedback.
- (iii) State **three** effects of negative feedback on an amplifier. (9 marks)

SECTION B: CONTROL SYSTEMS

Answer **TWO** questions from this section.

6. (a) A control system is described by the following open-loop expression.

$$G(s) = \frac{10(s+2)(s-4)}{s(s+1)(s+3)}$$

- (i) Determine the:
 - I. poles;
 - II. zeros.
- (ii) Sketch the poles and zeros on a s-plane.
- (iii) State with reasons the stability of the system. (9 marks)

- (b) A unity feedback system has an open-loop transfer function

$$G(s) = \frac{k}{s(s+10)}$$

- (i) Determine the:

- I. characteristic equation;
- II. value of k so that the system will have a damping ratio of 0.5.

- (ii) For this value of k determine, for a unit step input, the:

- I. settling time;
- II. percentage peak overshoot. (11 marks)

7. (a) With aid of block diagrams, describe each of the following:

- (i) transfer function;
- (ii) series compensation. (6 marks)

- (b) A signal flow graph is described by the following linear equations:

$$y = y_1 + \alpha U$$

$$\dot{y}_1 = -\beta y_1 + y_2 + \alpha_2 U$$

$$\dot{y}_2 = -\beta_2 y_1 + \alpha U$$

- (i) Determine the transfer function of the equations using Laplace transforms.

- (ii) Draw the signal flow diagram.

- (iii) Using Mason's rule, determine the transfer function of the system. (14 marks)

8. (a) State **two** advantages of servomotors over stepper motors with respect to control system. (2 marks)

- (b) A unity feedback control system is described by the open-loop transfer function:

$$G(s) = \frac{k}{s(s^2 + 2s + 2)(s^2 + 6s + 10)}$$

Determine each of the following with respect to root locus:

- (i) the zeros;
- (ii) the poles;
- (iii) centroid;
- (iv) asymptotic angles. (8 marks)

(c) Figure 4 shows a Nichols plot for a control system. Determine the:

- (i) phase margin;
- (ii) gain margin;
- (iii) peak value of closed-loop gain response, M_p ;
- (iv) resonant frequency;
- (v) bandwidth.

(10 marks)

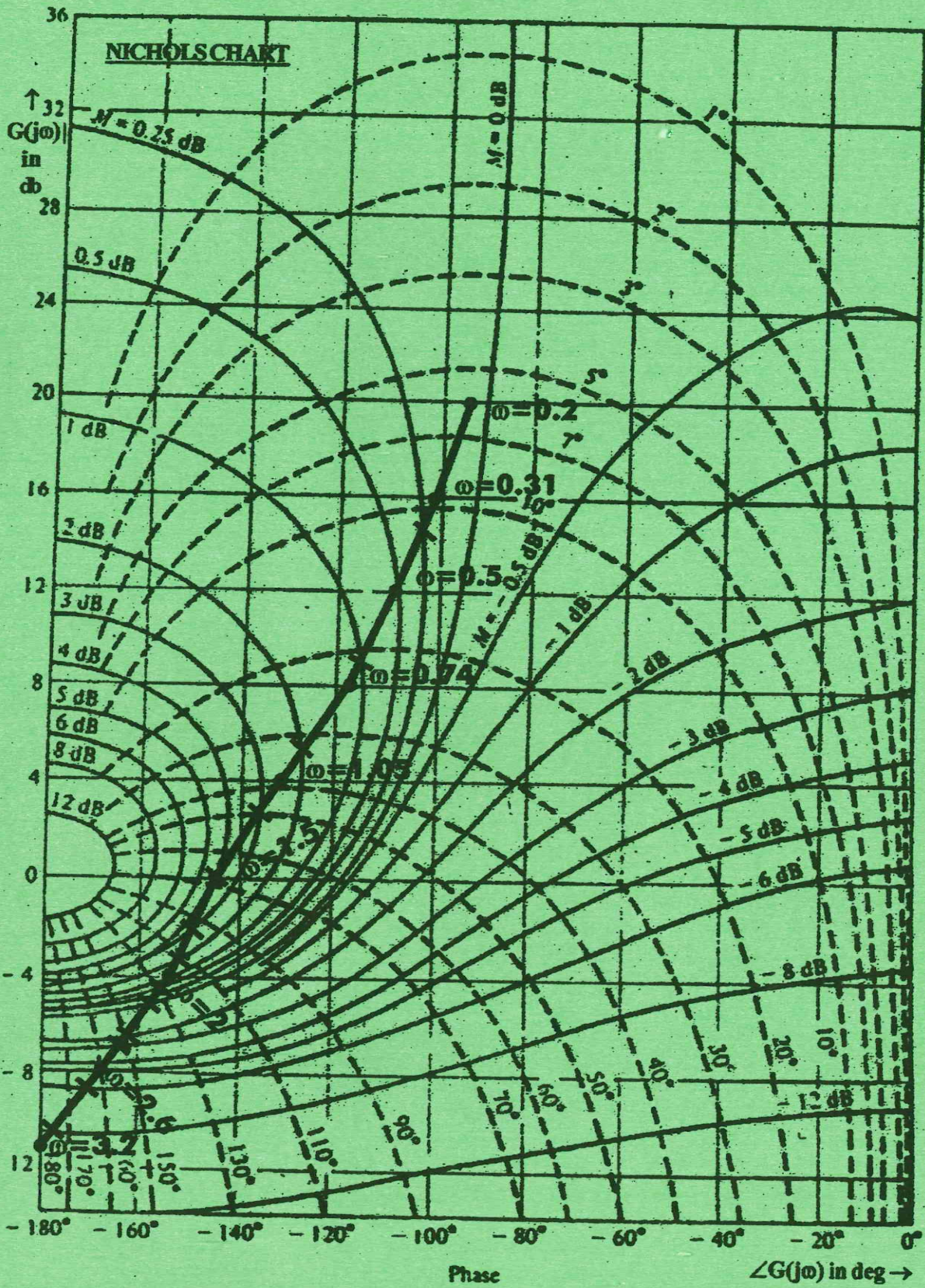


Fig. 4: Nichols plot of $G(j\omega)$

THIS IS THE LAST PRINTED PAGE.