



EAST AFRICAN SCHOOL OF AVIATION EXAMINATION

DIPLOMA IN AERONAUTICAL ENGINEERING AVIONICS

SUBJECT: ELECTRICAL CIRCUIT ANALYSIS

STREAM: Y2 Avionics

Duration:3.00 HRS

DAY/DATE: WEDNESDAY:05/04/1017

TIME: 2:00—5:00PM

INSTRUCTION TO CANDIDATES

1. This paper consists of **FOUR (4)** pages
2. You should have the following for this examination:
Answer booklet;
Mathematical tables/ Electronic calculator.
3. Answer FIVE questions

1. (a) Describe how phase voltage and line voltage are measured in a star connected 3-phase system. **(4 marks)**
 - (b) Calculate the line voltage of a 3 phase star connected system whose phase voltage is 240 volts. **(4 marks)**
 - (c) Explain how the magnitude of the line current is achieved in a delta connected system. **(6 marks)**
 - (d) Write down the formula of calculating the line voltage of a star connected 3 phase system and state how line voltage, phase, voltage, line current and phase current are related in a balanced delta connected system. **(6 marks)**

2. (a) State the laws of Kirchhoff's and calculate the current to a point(node) in an electrical circuit having three branches of +20 amperes,+2 amperes and -18 amperes. **(6 marks)**
 - (b) Define the meaning of the following in electrical circuits:
 - (i) Passive network
 - (ii) Bilateral circuit
 - (iii) Electric network
 - (iv) Non linear circuit **(8 marks)**
 - (c) Calculate the impedance of a series circuit consisting of a capacitor with a reactance of 7 ohms, an inductor with a reactance of 10 ohms and a resistor with resistance of 4 ohms. **(6 marks)**

3. Calculate the impedance, the current flow and the voltage drop in a series circuit with a capacitor of $200\mu\text{f}$ which is connected in series with a lamp of 10 ohms and a power supply of 110V AC 60cycles.Take π as 3.14 **(20 marks)**

4. (a) Explain how low pass filters are operating with well labeled diagrams of inverted L,T and π type. **(9 marks)**
 - (b) Describe how the output taken across the Capacitor will be if the inductive reactance (X_L) is small and the capacitive reactance (X_C) is large. **(2 marks)**
 - (c) State the purpose of High Pass filter and support the answer with three different types of inverted L,T and π diagrams. **(9 marks)**

5. (a) Name four types of LC Filters and explain what a filter is. **(5 marks)**
 - (b) Explain the reason why the filter networks are reactive. **(3 marks)**
 - (c) Define the meaning of the word "cut-off frequency(f_c)" **(2 marks)**
 - (d) With well labeled graphs of ideal characteristics of low pass filter and high pass filter show attenuation, frequency , frequency cut off, pass band and stop band. **(10 marks)**

6. (a) Describe how the lines and phases of delta and star are connected, and show the formulae of calculating the voltages, and currents in the circuits. **(6 marks)**

- (b) State the difference between a three phase star three wire connected system and a three phase star four wire connected system . **(4 marks)**
- (c) Calculate the value of the impedance and total current flow in a circuit connected to a generator of 110V AC 60cycles and a load of $2\mu\text{f}$ capacitance and a 10,000 ohms resistance in parallel. Take π as 3.14. **(10 marks)**
7. (a) State the function of each of the following parts of a DC machine
 (i) Field system
 (ii) Armature winding
 (iii) Commutator **(6 marks)**
- (b) Describe armature reaction and with a well labeled diagram, show how interpoles are used to correct the reaction. **(14 marks)**
- 8 (a) Explain why transformers are rated in Volt-Amperes (VA) instead of watts(W) **(3 marks)**
- (b) Draw a circuit of a delta –star connection of three phase transformer and explain two advantages of this transformer connection. **(9 marks)**
- (c) The iron loss and full load copper loss in a 50 KVA transformer is 500 W and 800W respectively. If the power factor is 0.8 lagging, determine the efficiency at;
 (i) half load
 (ii) full load **(8 marks)**
- (b) (i) Explain two (2) groups of capacitors and from each group write two kinds of capacitors. **(6 marks)**
- (ii) Clearly write down the formulae used for capacitors in series and parallel and calculate the total capacitance of three capacitors of values of $10\mu\text{f}$, $5\mu\text{f}$ and $8\mu\text{f}$ which are connected in series. **(6 marks)**
9. A lamp of 6 ohms and an inductor of 0.021henrys are connected in series to a power supply of 110V AC 60cycles. Calculate:
 (a) The current flow **(8 marks)**
 (b) The voltage drop across the resistance and across the inductance. **(4 marks)**
 (c) Prove that the voltage drops is equal to the power supply. **(8 marks)**
- 10 (a) Describe True Power and Apparent Power and calculate the apparent power and the power factor where a 220 VAC motor takes 50 Amperes from the line ,but the wattmeter in the line shows that only 9350 watts are taken by the motor. **(14 marks)**
- (b) With a well labeled diagram, show the power relations in AC circuits. **(6 marks)**

11. (a) (i) Define armature reaction and explain how this reaction can be counteracted. **(4 marks)**
- (ii) Name two types of armatures which are currently in existence. **(2 marks)**
- (ii) Explain how generators are rated and state where this information of generator rating can be found on a generator. **(2 marks)**
- (b) Show the generator characteristics of series connection, shunt connection, differential compounding and cumulative compounding in a well labeled diagram taking X axis from 0-100% current output and Y axis from 0-100% voltage output. **(12 marks)**
- 12 (a)(i) Explain the principle of operation of an AC single phase motor when used as a capacitor start and state why the centrifugal switch is connected in series with the capacitor in the starting winding. **(6 marks)**
- (ii) Describe how motor speeds are controlled. **(4 marks)**
- (b) In a well labeled diagram of a load characteristic of a DC motor show series connection, cumulative compounding, shunt connection and differential compounding taking X axis output power or load from 0-100% and Y axis as speed of rotation from 0 -100%. **(10 marks)**
13. (a) Explain the four(4) major parts of a DC machine. **(6 marks)**
- (b) State where split phase and capacitor start motors can be used. **(4 marks)**
- (c) Describe the purpose of an equipment rating or name plate. **(2 marks)**
- (d) Explain how DC machines are classified. **(8 marks)**
14. (a) Calculate the line voltage of a 3 phase star connection system which has a phase voltage of 240v and explain how phase voltage and line voltage are measured. **(10 marks)**
- (b) Describe which line is always used as the return in a Delta connection 3 phase distributor and explain how line voltage and phase voltage are the same and line current is 3 times the phase current. **(10 marks)**
15. (a) (i) Name and describe three major parts of a transformer.
- (ii) Explain how power is coupled to secondary winding from primary winding. **(2marks)**
- (iii) In transformer, explain turns ratio. **(2 marks)**
- (b) (i) Define transformer efficiency and give its units. **(3 marks)**
- (ii) Name all the losses of transformer and explain how they can be reduced **(4 marks)**
- (iii) Explain how transformers are rated. **(3 marks)**