



**EAST AFRICAN SCHOOL OF AVIATION
EXAMINATION**

END TERM I

ENGINEERING SECTION

SUBJECT: MICRO CONTROLLER TECHNOLOGY

STREAM: Module III (AVIONICS)

Duration: 2HRS 30 mins

DAY/DATE: 3rd April 2017

TIME: 9Am – 12Pm

INSTRUCTION TO CANDIDATES

- 1. Answer any ALL questions*
- 2. Maximum marks for each part of a question are as shown*

1. a) Explain why binary number system is employed in digital systems (2 marks)
- b) Fill the conversion table below and show all the workings.

Decimal	Binary	Octal	Hexadecimal
		753.6	
			3EB
563.2			
	10111100111101		

(12 marks)

- c) The number CAB_{16} is a two byte. Determine its decimal value if it is in
 I. Ones's complement
 II. Two's complement (6 marks)
- 2 a) (i) Evaluate the following, showing all the working
 I. $BEBC_{16} - 94EF_{16}$ (4 marks)
- (ii) Use 8-bit 2's complement arithmetic to evaluate $(-37_{10}) - (69_{10})$ (5 marks)
- (iii) For the one byte number, 10011101_2 , determine its decimal value if it is in
 I. One's complement
 II. Two's complement
 III. Unsigned (6 marks)
- b) State three methods used to represent negative numbers (3 marks)
- c) State two advantages of using hexadecimal over binary number systems (2 marks)
- 3 a) (i) Define a canonical term. Distinguish between a maxterm and a minterm (4 marks)
- (ii) Obtain the standard sum of products (SSOP) form of the following Boolean function
 $F = AB + ACD' + B'D$ (5 marks)
- b) For the following Boolean function

$$F(A,B,C,D) = \Sigma (0,1,2,3,7,8,9,12,14)$$

- i Draw the truth table
 - ii Draw a K-map representation of the function
 - iii Simplify and state the output function as a sum of products
 - iv Implement the simplified circuit (11 marks)

- 4 a) A function F is defined such that it equals logic 1 when a 4 bit input code is equivalent to any of the decimal numbers 3,6,9,12 or 15. F is logic 0 input codes 0,2,8 and 10. F is indeterminate for other input values
 - i Use a truth table and Karnaugh map to determine the minimal expression for this function

 - ii Implement the minimal expression using
 - I. NAND gates
 - II. NOR gates (14 marks)

- b) use the Boolean algebra postulates and theorems to minimize the following expressions
 - i $XYZ + X'YZ' + X'YZ + XYZ' + X'Y'Z'$
 - ii $AB + CB' + CAB + ABD$ (6 marks)

- 5 a) State the difference between sequential logic circuit and combinational logic circuits giving an example of each. (2 Marks)

- b) Using suitable expressions and truth table implement a 1-bit digital comparator (5 marks)

- c) With the aid of a truth table and logic expressions, implement a 4-to-line multiplexer (data selector) (4 Marks)

- d) Perform the following binary arithmetic
 - i. $1011011 + 1011110$
 - ii. $1011 - 1101$ using two's complement method
 - iii. $1100 - 10001$ using one's complement (9 marks)